
 



1947 Point Contact transistor

 


Source: Bell Labs



1961 Fairchild Bipolar RTL RS Flip-Flop

 


Source: Fairchild

 


Moore's Law (1965) Number of components has doubled every year and will continue to do so until 1975

 Moore's Law (1975) Number of components will double every two years




Self-fulfilling
Prophecy


RTL NOR Gate

 


TTL NAND Gate

 



ECL OR/NOR Gate

 

NMOS Compound Gate

 

CMOS Compound Gate

  

- Bipolar Transistors with Resistors - MSI/LSI

RTL - NOR

TTL - NAND

ECL - OR/NOR


- MOS Transistors (no resistors) - VLSI

NMOS


CMOS - No static power!

Both allow construction of NOR, NAND & Compound gate (always inverting)


Diode

 


NPN Transistor

 



NMOS Enhancement transistor
NMOS Process

 


Resistor

 


Capacitors

  

PMOS Enhancement transistor
CMOS Process

 

Active Area

 

Polysilicon




P+ Implant



N+ Implant




CMOS Inverter

 


Twin Tub CMOS Process

CMOS Inverter

 

N-Well CMOS Processes (with explicit N+ implant mask)


CMOS Inverter

 


N-Well CMOS Processes (without explicit N+ implant mask)

Features may be determined by a number of masks
e.g. NMOS source drain: ActiveArea AND NOT(NWell OR Poly OR PImplant)

 
Design Rules – width, separation, overlap



Optimised Mask Layout


 


Equivalent Stick Diagram

 

- Metal
- Polysilicon
- N+
- P+
- Contact
- Tap
- Combined contact & tap

  
Investigation of Euler paths leads to more efficient layout*




*not all gates will support a common Euler path for both PMOS and NMOS

1 METAL LAYER



LAYOUT

 





ABSTRACT

 






ROUTING

  


2 METAL LAYERS

    



3 METAL LAYERS

     



Pass Transistor

 

CMOS Transmission Gate

  

Transmission Gate Multiplexor

  


*note distinctive polysilicon crossover


Tri-state gates are used for Multiplexing

Distributed Multiplexing


using transmission gates

 




using tri-state inverters

 



using tri-state buffers

 


Tri-state Inverter

   

Tri-state Buffer



 
 


Bi-directional I/O




 


*this is another form of multiplexing

Latch

    


Master Slave D-Type Flip-Flop

    


*multiplexor based latches and flip-flops include distinctive polysilicon crossover

Edge Triggered D-Type Flip-Flop

 


26 Transistors

 


Euler path analysis is applied creatively to these multi-gate cells – gates are often linked via the common gnd/pwr node
Final layouts will be more complex where clock buffers, reset circuitry and metal 2 i/o are included

PLA and ROM

 


ROM is PLA with
fixed AND (decoder) plane
programmable OR (data) plane

SRAM

 

Cells are designed to butt together in two dimensions leading to efficient layout

 PLA layout efficiency will depend on the actual function implemented (e.g. number of common product terms)



All design styles need full custom designers

A large ASIC (especially SoC) may mix Semi-Custom and Full Custom