
PLA structures

 
Programmable Logic Array structures provide a logical and compact method of implementing multiple SOP (Sum of Products) or POS expressions.



Most PLA structures employ pseudo-NMOS NOR gates using a P-channel device in place of the NMOS depletion load.


PLAs, ROMs and RAMs



 


- Unlike complementary CMOS circuits, these gates will dissipate power under static conditions (since the P device is always on).
- The P and N channel devices must be ratioed in order to create the required low output voltage.
- This ratioing results in a slower gate, although there is a trade-off between gate speed and static power dissipation.

PLAs, ROMs and RAMs

 


• A regular layout is employed, with columns for inputs and outputs and rows for intermediate expressions.

PLA structure

 

 
• Layout is simply a matter of selecting and placing rectangular cells from a limited set.



• Conversion to *sticks* is straight forward with opportunities for further optimization.

ROMs

 • A ROM may simply be a PLA with fixed decode plane¹ and programmable data plane.




¹RAM structures can make use of the same decode plane.

PLAs, ROMs and RAMs


Static RAM

 - Used for high density storage on a standard CMOS process.
- Short lived conflict during write NMOS transistors offer stronger path.
- Differential amplifiers are used for speedy read.




Standard 6 transistor static RAM cell.

SRAM Structure

 

10008

SRAM Write

 

SRAM Write

