

Synchronous Systems

 


- All parts of the system share the same clock and the same clock edge sensitivity.
- The data may change between active clock transitions but must be stable by the time the next active transition occurs¹.

¹for most systems the *active transition* is the rising edge of the clock

Synchronous Systems - D-type Timing

 

 - Valid data should be present on D input for at least t_{setup} before the active clock edge and at least t_{hold} after the clock edge.
- The minimum D-type cycle time will be limited by the sum $t_{setup} + t_{pQ}$.



• To avoid a setup violation:

$$ClockPeriod > t_{pQ} + t_{comb} + t_{setup}$$

• To avoid a hold violation:


$$t_{pQ} + t_{comb} > t_{hold}$$

Static Timing Analysis

- Predicts the timing of a circuit without simulation²
- Analysis of gate network based on:
 - Propagation delays
 - Set-up and hold times for storage elements
 - Constraints such as desired operating frequency and the timing of inputs and outputs

Note that the examples given here are simplified in that they reduce the propagation delay through a gate to a single number - in reality there are predictable and unpredicatble variations in gate delays which must be accounted for by static timing analysis tools.

 ²timing simulations for large digital systems are slow and will usually not catch all edge and coner cases




• To avoid a setup violation:

$$ClockPeriod > t_{pQ} + t_{comb-max} + t_{setup}$$

• To avoid a hold violation:


$$t_{pQ} + t_{comb-min} > t_{hold}$$

 

• Critcal path analysis allows us to determine the maximum feasible clock frequency:

$$ClockPeriod > t_{pQ} + t_{comb-max} + t_{setup}$$

 
$$f_{max} = \frac{1}{t_{pQ} + t_{comb-max} + t_{setup}}$$



$$t_{pQ} + t_{comb-min} > t_{hold}$$

If we have an ideal clock and $t_{pQ} > t_{hold}$ we won't see hold violations even with if $t_{comb-min} = 0$.

Synchronous Systems - Clock Skew

 


• Clock Distribution

The process of distributing clocks from a central source gives rise to delays. **Clock skew** is the difference between the arrival times of the clock at different points in the circuit.

Clock Skew may cause unexpected timing violations

Hold: if *D-type* #1 clocks first, D input of *D-type* #2 may change too early³ **Setup:** if *D-type* #1 clocks second, D input of *D-type* #2 may change too late

 ³most likely where combinational logic is minimal or absent




• To avoid a setup violation:

$$ClockPeriod > t_{pQ} + t_{comb} + t_{setup} + (t_{d1} - t_{d2})$$

• To avoid a hold violation:
 
$$t_{pQ} + t_{comb} > t_{hold} + (t_{d2} - t_{d1})$$




• What is the maximum operating frequency of the circuit if the clock skew is no more than 16ps?

$$ClockPeriod > t_{pQ} + t_{comb} + t_{setup} + t_{skew}$$

• What is the maximum clock skew that can be tolerated before we have a hold violation?

$$t_{pQ} + t_{comb} > t_{hold} + t_{skew}$$


Critical Path

 

• To avoid a setup violation:

$$ClockPeriod > t_{pQ} + t_{comb-crit} + t_{setup} + t_{skew}$$


Critical Path

 

• To avoid a setup violation:

$$ClockPeriod > t_{pQ} + t_{comb-crit} + t_{setup} + (t_{d1} - t_{d4})$$


Critical Path

 


$$ClockPeriod > t_{pQ} + t_{comb-crit} + t_{setup} + (t_{d_{launch}} - t_{d_{capture}})$$

• If we can control the skew (e.g. by increasing t_{d4}), we can ease the timing constraint.⁴

 
⁴this may result in the critical path moving to another part of the circuit



 
• Calculate f_{max} in the presence of intentional clock skew.



 
- Calculate f_{max} in the presence of intentional clock skew.
- Suggest suitable values for t_{d1} , t_{d2} , t_{d3} , t_{d4} , t_{d5} , t_{d6}



 - ullet Calculate f_{max} in the presence of intentional clock skew.
- Suggest suitable values for t_{d1} , t_{d2} , t_{d3} , t_{d4} , t_{d5} , t_{d6} Initially set all to a minimum value (in this case 50ps)



 
- Calculate f_{max} in the presence of intentional clock skew.
- Suggest suitable values for t_{d1} , t_{d2} , t_{d3} , t_{d4} , t_{d5} , t_{d6}
- ⇒ Identify longest timing paths



- Calculate f_{max} in the presence of intentional clock skew.
- Suggest suitable values for t_{d1} , t_{d2} , t_{d3} , t_{d4} , t_{d5} , t_{d6}
- ⇒ Identify longest timing paths


$$t_{path} = t_{pQ} + t_{comb} + t_{setup} + (t_{d_{launch}} - t_{d_{capture}})$$

$$20018$$

 


$$ClockPeriod > t_{pQ} + t_{comb-A} + t_{setup} + (t_{d1} - t_{d4})$$
 
$$f_{max} = \frac{1}{t_{pQ} + t_{comb-A} + t_{setup} + (t_{d1} - t_{d4})}$$




$$ClockPeriod > t_{pQ} + t_{comb-crit} + t_{setup} + (t_{d_{launch}} - t_{d_{capture}})$$
 
$$f_{max} = \frac{1}{t_{pQ} + t_{comb-crit} + t_{setup} + (t_{d_{launch}} - t_{d_{capture}})}$$




  \Rightarrow Initially try increasing t_{d4} by 20ps




$$ClockPeriod > t_{pQ} + t_{comb-crit} + t_{setup} + (t_{d_{launch}} - t_{d_{capture}})$$
 
$$f_{max} = \frac{1}{t_{pQ} + t_{comb-crit} + t_{setup} + (t_{d_{launch}} - t_{d_{capture}})}$$



$$ClockPeriod > t_{pQ} + t_{comb-crit} + t_{setup} + (t_{d_{launch}} - t_{d_{capture}})$$

 
$$f_{max} = \frac{1}{t_{pQ} + t_{comb-crit} + t_{setup} + (t_{d_{launch}} - t_{d_{capture}})}$$



- Calculate f_{max} in the presence of intentional clock skew.
- Suggest suitable values for t_{d1} , t_{d2} , t_{d3} , t_{d4} given that the minimum delay through the clock tree is 50ps

remember to check for hold violations

Synchronous Systems - Jitter

 


- Jitter

 Jitter is the cycle-by-cycle variation in the arrival time of the clock.
- Caused by
 - Variation in frequency/phase of clock source⁵
 - Power supply noise affecting clock distribution
 - Cross-talk affecting clock distribution
- Jitter may cause unexpected timing violations

⁵primary clock source or Phase-Locked Loop (PLL)

Synchronous Systems - Jitter

 


• To avoid a setup violation:

$$ClockPeriod > t_{pQ} + t_{comb} + t_{setup} + (t_{d1} - t_{d2}) + 2 \times t_{jitter}$$

• To avoid a hold violation:

$$t_{pQ} + t_{comb} > t_{hold} + (t_{d2} - t_{d1}) + 2 \times t_{jitter}$$

 Synchronous Systems - Static Timing Analysis (skew + jitter)



• What is the maximum jitter that can be tolerated given an operating frequency of 6GHz and clock skew of no more than 16ps?⁶

$$ClockPeriod > t_{pQ} + t_{comb-max} + t_{setup} + t_{skew} + 2 \times t_{jitter}$$

$$t_{pQ} + t_{comb-min} > t_{hold} + t_{skew} + 2 \times t_{jitter}$$

⁶remember to consider both setup and hold violations