

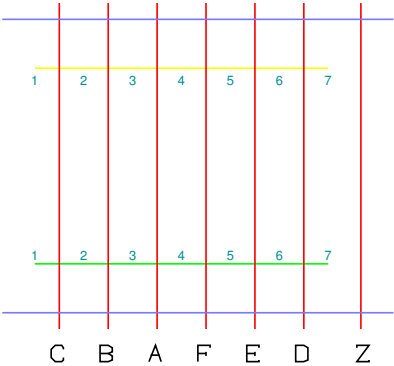


Finding an Euler Path

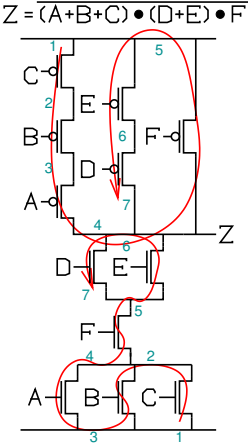

6008

Finding an Euler Path

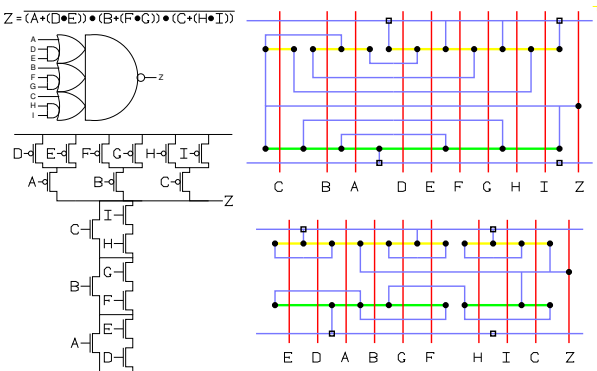

No possible path through p-transistors.
No re-arrangement will create a solution!

6009