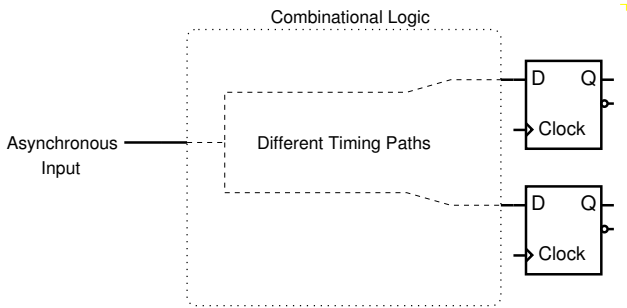


# Synchronous Systems

## Asynchronous Inputs




With different timing paths through combinational logic, we can get unexpected results.

21001

# Synchronous Systems

## Asynchronous Inputs

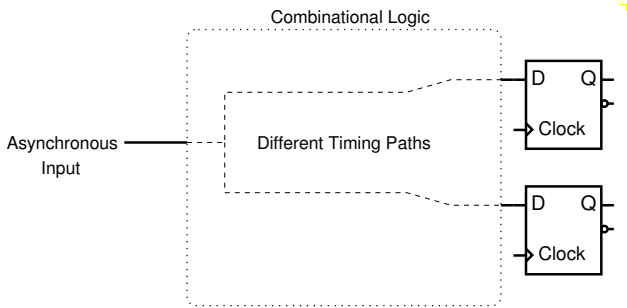


Retiming the asynchronous input before the combinational logic block should give more predictable results.

21003

# Synchronous Systems

## Asynchronous Inputs

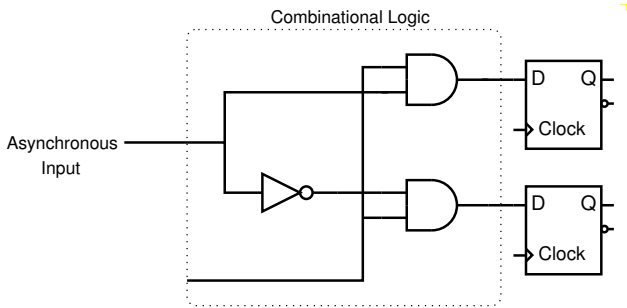


With different timing paths through combinational logic, we can get unexpected results.

*In this example, a falling input we may be registered as neither high nor low.*

21002

# Synchronous Systems


## Asynchronous Inputs

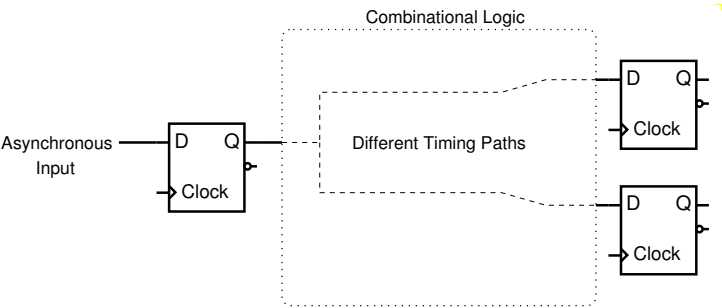

Retiming the asynchronous input before the combinational logic block should give more predictable results.

21004

## Asynchronous Inputs

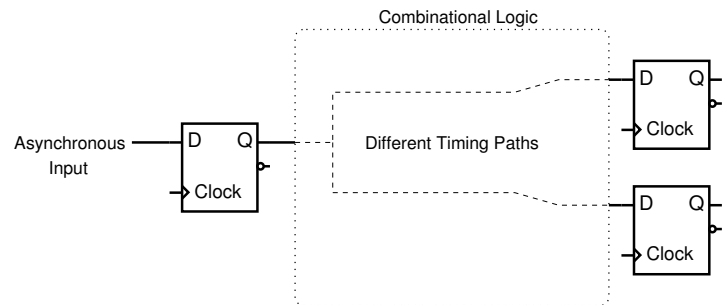

To avoid a setup violation<sup>1</sup>:

$$ClockPeriod > t_{pQ} + t_{critical\_path} + t_{setup}$$


---

<sup>1</sup>assuming ideal clock

21005

## Synchronous Systems

## Asynchronous Inputs

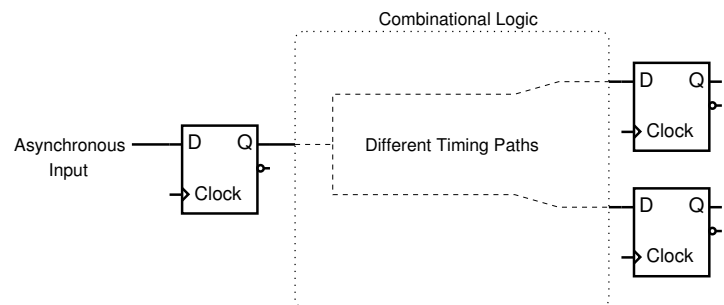

To avoid a setup violation<sup>1</sup>:

$$ClockPeriod > t_{pQ} + t_{critical\_path} + t_{setup}$$


but  $t_{pQ}$  may now be unpredictable

<sup>1</sup>assuming ideal clock

21006

## Synchronous Systems
 
### $t_{pQ}$ Variation with Late Arriving Data




- As the setup time ( $t_{setup}$ ) is reduced (close to its absolute minimum value), the clock-to-Q delay ( $t_{pQ}$ ) increases sharply.
- A flip-flop datasheet will quote a  $t_{pQ}$  value for a minimum  $t_{setup}$  value. When we violate the minimum specified  $t_{setup}$  value, the quoted  $t_{pQ}$  value is no longer valid.

21007

## Synchronous Systems

## Asynchronous Inputs

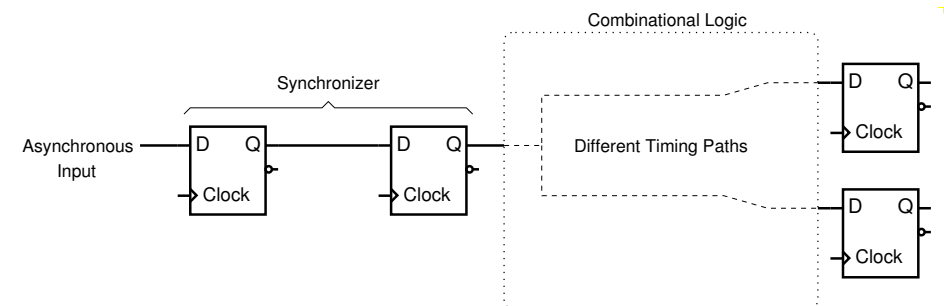


A second flip-flop in the synchronizer gives a predictable  $t_{pQ}$  for our equation:

$$ClockPeriod > t_{pQ} + t_{critical\_path} + t_{setup}$$

21008


## Flip-Flop Stable States

 

The third state is described as *metastable* since a slight perturbation in one of the 50%-of- $V_{DD}$  voltages will result in a move to one of the other states.

21009

## Metastability

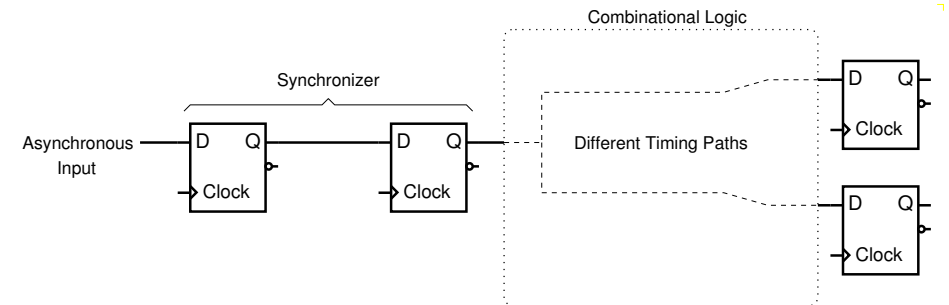

- The first flip-flop in our synchronizer may go metastable in the extreme case where the set-up time for D is reduced and  $t_{pQ}$  increases.
- The two flip-flop synchronizer gives a full clock cycle for the metastable state to resolve itself into one or other normal state.

21010