

• Static

After the appropriate propagation delay the ouput becomes valid and remains valid.¹


• Complementary

For any set of inputs there will exist either a path to Vdd or a path to GND.

Where this condition is not met we have either a high impedence output or a conflict in which the strongest path succeeds. Static CMOS **Non-complementary** gates make use of these possibilities.

¹c.f. Dynamic logic which uses circuit capicitance to store state for a short time.

• Pass Transistor

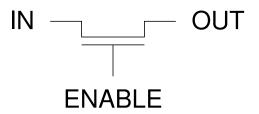


- Provides very compact circuits.

- Good transmission of logic '0'.
- Poor transmission of logic '1'.
 - - slow rise time
 - - degradation of logic value

The pass transistor is used in many dynamic CMOS circuits².


²where pull-up is performed by an alternative method

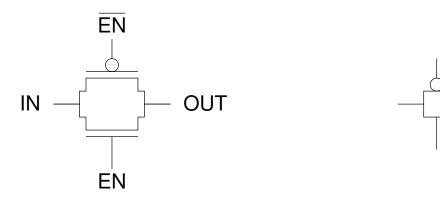- Transmission Gate
 - For static circuits we would normally use a CMOS transmission gates:



- - balanced *n* and *p* pass transistors
- - faster pull-up
- - slower pull-down


• Transmission Gate Layout

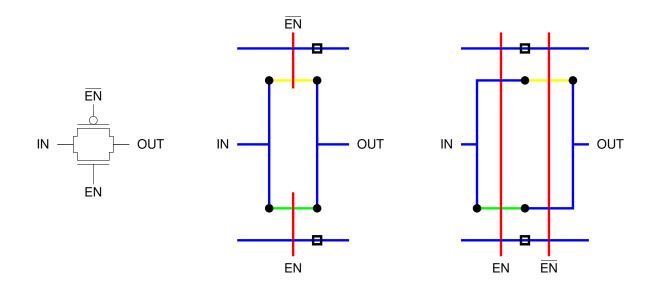

note that these circuits are not fully complementary³ hence they do not immediately lend themselves to a *line of diffusion* implementation.


³since there are sets of inputs for which the output is neither pulled low nor high

• Transmission Gate Multiplexor

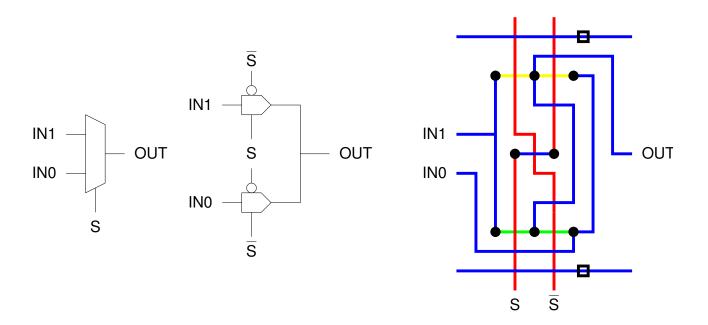

- very few transistors 4 (+2 for inverter)
- difficult layout may offset this advantage
 - - prime candidate for 2 level metal


• Bus Wiring

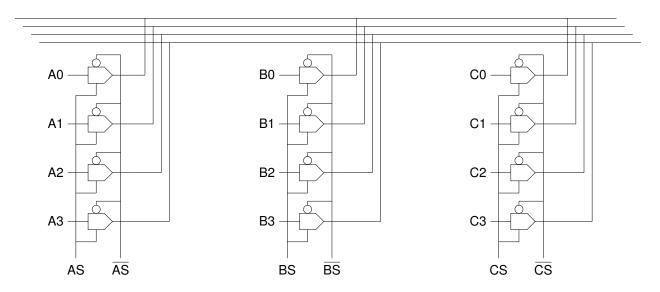

- distributed multiplexing⁴
- only one inverter required per bank of transmission gates
- greatly simplifies global wiring


⁴internal chip bus should never be allowed to float high impedance

Bus Distributed Multiplexing

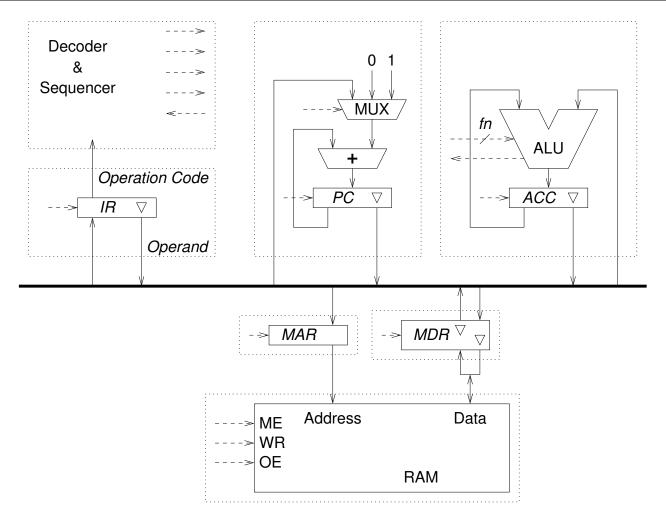


Ideal for signals with many drivers from different modules.

8007

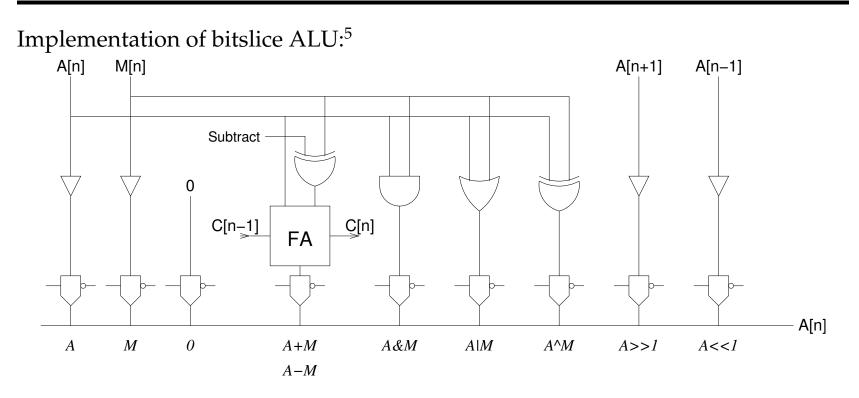


- Separate circuit for each function
- Connected via distributed multiplexor

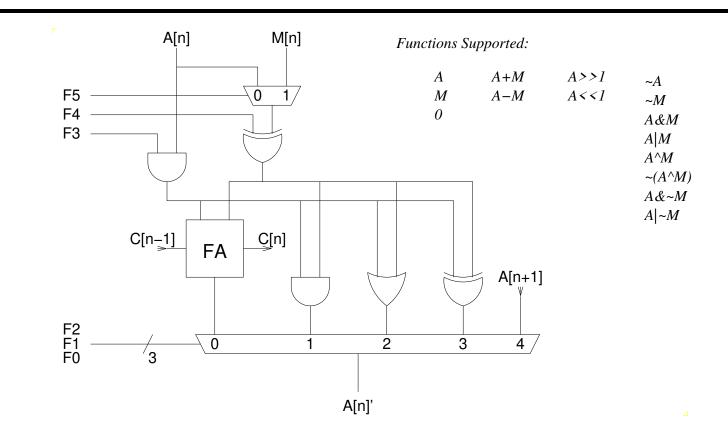⁵Note that transmission gates have no drive capability in themselves. Here a good drive is ensured by providing buffers.




- Single optimized ALU module
- Multiplexing is not distributed
- Multiplexor implementation may use transmission gates

• Tristate Inverter

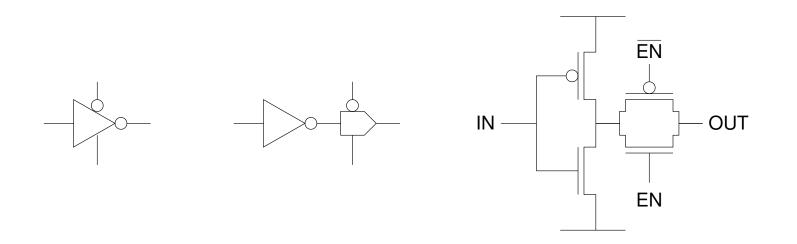


 Any gate may have a tri-state output by combining it with a transmission gate.

• Tristate Inverter

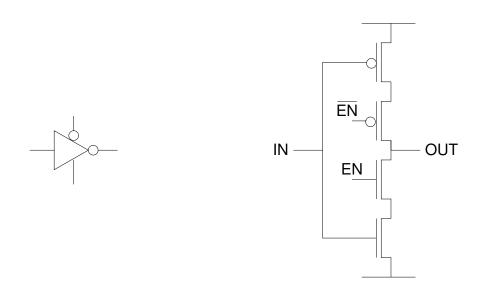


- Alternatively the transmission gate may be incorporated into the gate.
 - - one connection is removed easier to layout
 - - also easier to simulate!

• Tristate Inverter Layout

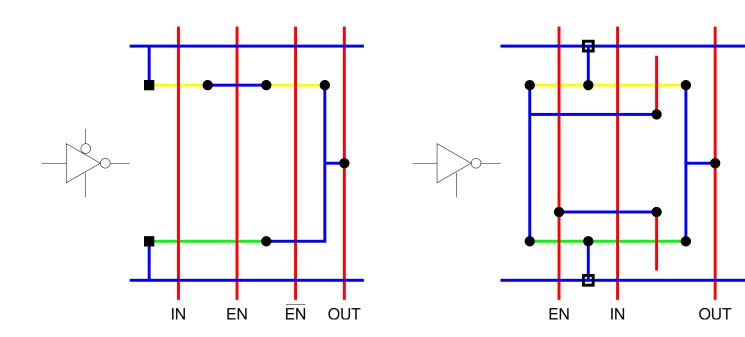

• Tristate Inverter Bus Driver

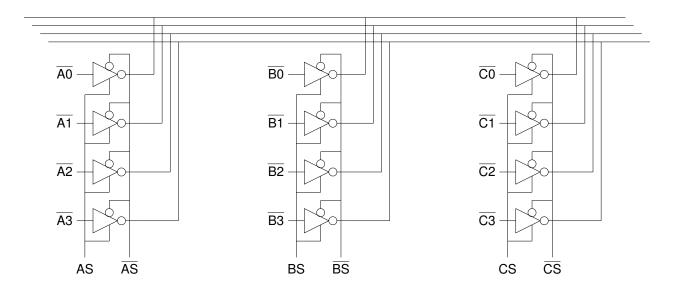

- a tristate inverting buffer is often used to drive high capacitance bus signals
- transistors may be sized as required

