 


PLAs, ROMs and RAMs

PLA structures


Programmable Logic Array structures provide a logical and compact method of implementing multiple SOP (Sum of Products) or POS expressions.



Most PLA structures employ pseudo-NMOS NOR gates using a P-channel device in place of the NMOS depletion load.

PLAs, ROMs and RAMs


Pseudo-NMOS NOR gate

 

- Unlike complementary CMOS circuits, these gates will dissipate power under static conditions (since the P device is always on).
- The P and N channel devices must be ratioed in order to create the required low output voltage.
- This ratioing results in a slower gate, although there is a trade-off between gate speed and static power dissipation.

PLAs, ROMs and RAMs


PLA structure

 

- A regular layout is employed, with columns for inputs and outputs and rows for intermediate expressions.

PLAs, ROMs and RAMs


PLA structure

 

- Layout is simply a matter of selecting and placing rectangular cells from a limited set.

PLAs, ROMs and RAMs

PLA structure

 


Only AND plane cells are shown here

- Conversion to *sticks* is straight forward with opportunities for further optimization.

PLAs, ROMs and RAMs

ROMs

 - A ROM may simply be a PLA with fixed decode plane¹




¹RAM structures can make use of the same decode plane.

PLAs, ROMs and RAMs

ROMs

 - A ROM may simply be a PLA with fixed decode plane¹




¹RAM structures can make use of the same decode plane.

PLAs, ROMs and RAMs

ROMs

 - A ROM may simply be a PLA with fixed decode plane¹ and programmable data plane.




¹RAM structures can make use of the same decode plane.

PLAs, ROMs and RAMs

ROMs

 - A ROM may simply be a PLA with fixed decode plane¹ and programmable data plane.




¹RAM structures can make use of the same decode plane.

PLAs, ROMs and RAMs

ROMs

 - A ROM may simply be a PLA with fixed decode plane¹ and programmable data plane.




¹RAM structures can make use of the same decode plane.

PLAs, ROMs and RAMs


Static RAM

 - Used for high density storage on a standard CMOS process.
- Short lived conflict during write - NMOS transistors offer stronger path.
- Differential amplifiers are used for speedy read.




Standard 6 transistor static RAM cell.

SRAM Structure

 


10008

SRAM Write


 


SRAM Write

 




10010

PLA and ROM

  

ROM is PLA with
 fixed AND (decoder) plane
 programmable OR (data) plane

SRAM

   

Cells are designed to butt together in two dimensions leading to efficient layout

PLA layout efficiency will depend on the actual function implemented (e.g. number of common product terms)