 



Transmission Gate



Note that transmission gate circuits are not fully complementary¹ hence they do not immediately lend themselves to a *line of diffusion* implementation.

¹since there are sets of inputs for which the output is neither pulled low nor high



Transmission Gate Multiplexor

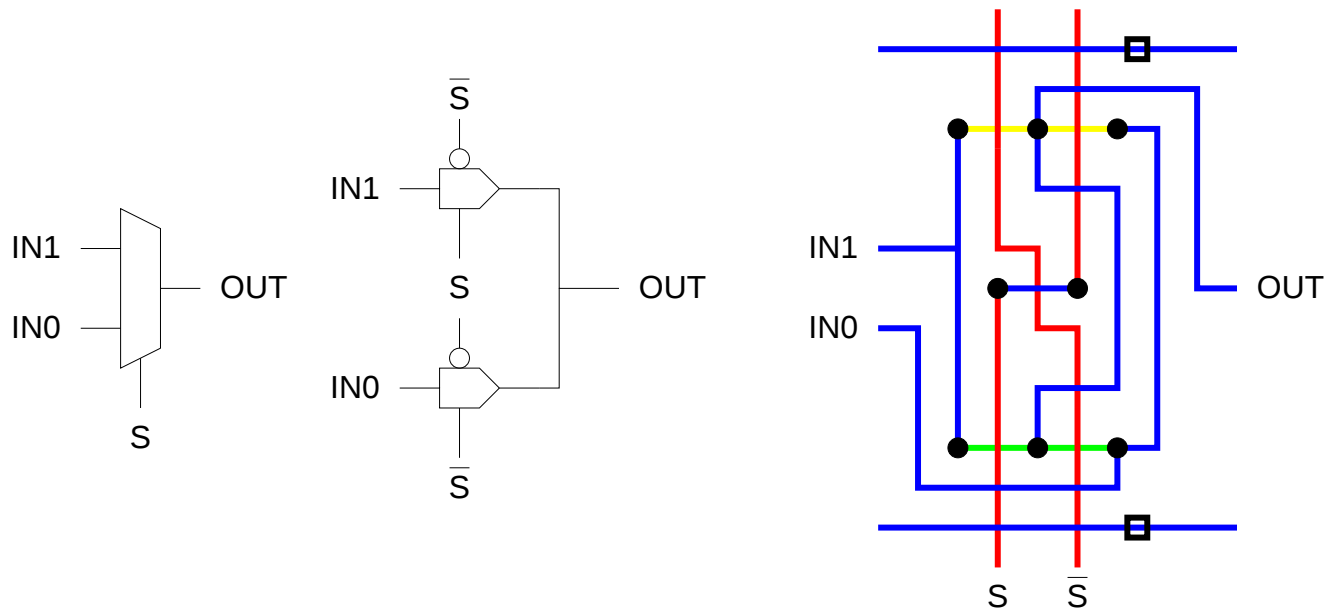

- very few transistors 4 (+2 for inverter)
- difficult layout may offset this advantage
 - prime candidate for 2 level metal

Storage elements

- CMOS transmission gate latch

 
 


A simple transparent latch can be build around a transmission gate multiplexor

- transparent when load is high
- latched when load is low
- two inverters are required since the transmission gate cannot drive itself

Storage elements



- Transmission gate latch layout

 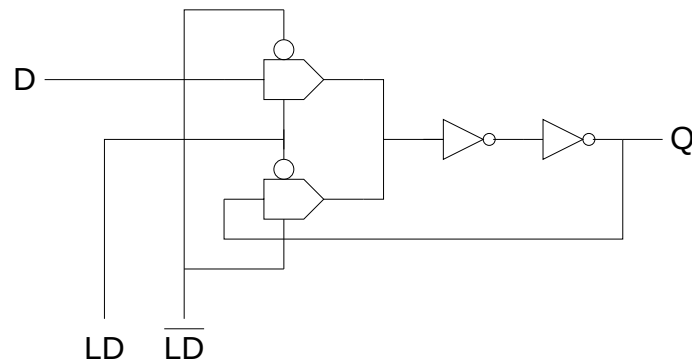

- a compact layout is possible using 2 layer metal

Storage elements

  
- A simpler layout may be achieved using tristate inverters.



- this design requires two additional transistors but may well be more compact.

Storage elements

 
- For use in simple synchronous circuits we use a pair of latches in a master slave configuration.




- this avoids the race condition in which a transparent latch drives a second transparent latch operating on the same clock phase.
- the circuit behaves as a rising edge triggered D type flip-flop.

Storage elements

- Transmission gate implementation

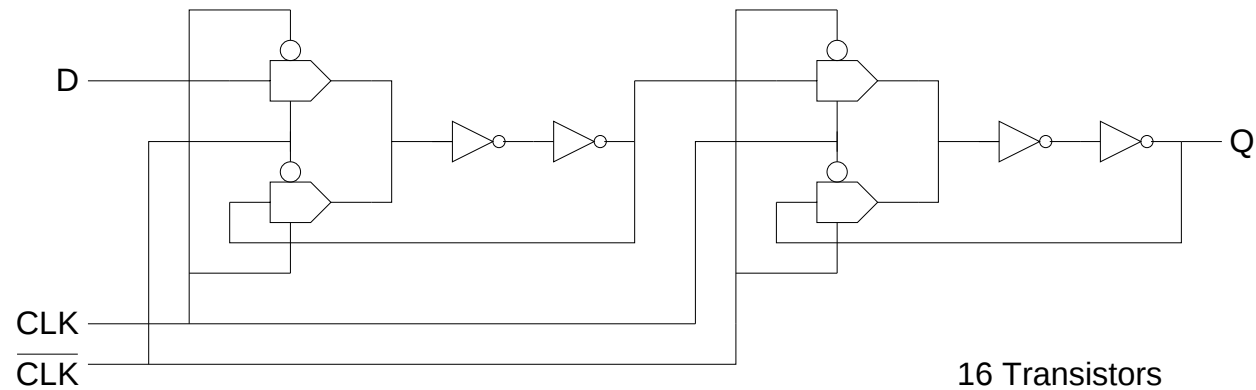


- Tristate inverter implementation

 


Storage elements

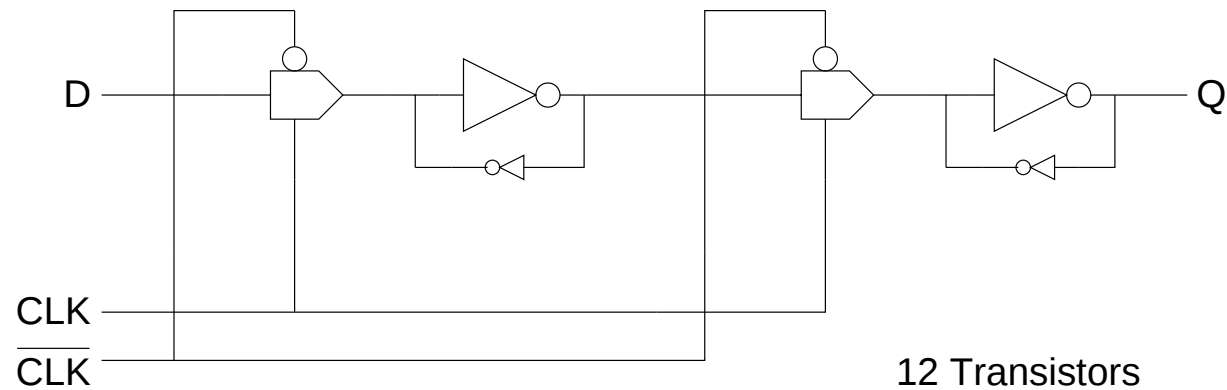- Transmission gate implementation using keepers




 - Tristate inverter implementation using keepers




Storage elements

- Alternative configuration


 


- Implementation

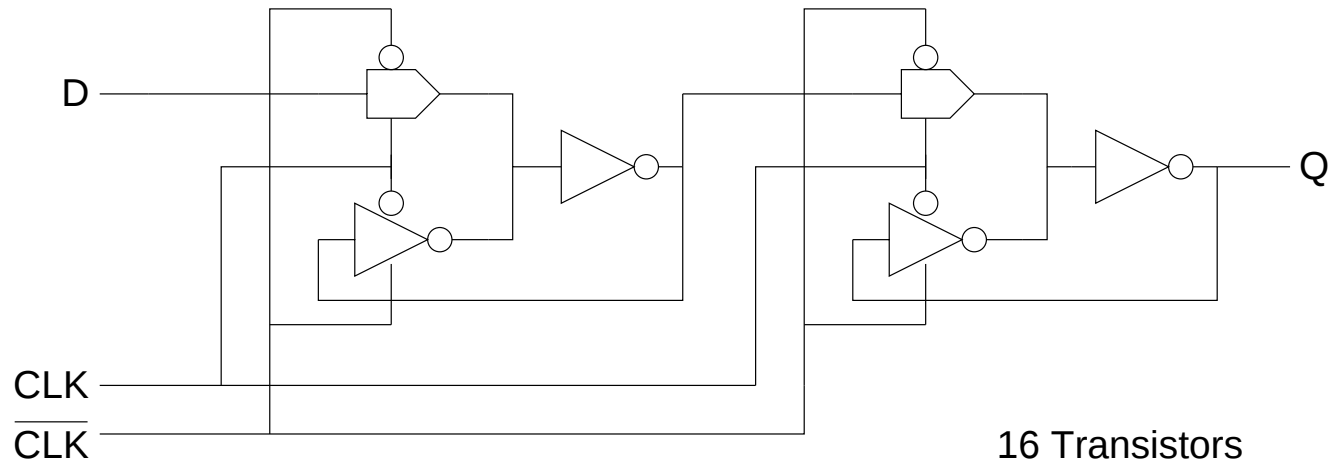

Storage elements


- Layout of master slave D type.

  

- very compact using alternative configuration.


Storage elements

 - For the same functionality we could use an edge triggered D type:



- a few more transistors
- more complex wiring
- simpler clock distribution

Edge Triggered D-Type with Reset (DFFR)

 

Master Slave D-Type with Reset (MSDR)

