 


# D type Timing

---


- Timing



- Valid data should be present on D input for at least  $T_s$  before the active clock edge and at least  $T_h$  after the clock edge.
- The minimum D type cycle time will be limited by the sum  $T_s + T_q$ .

# D type Timing

---

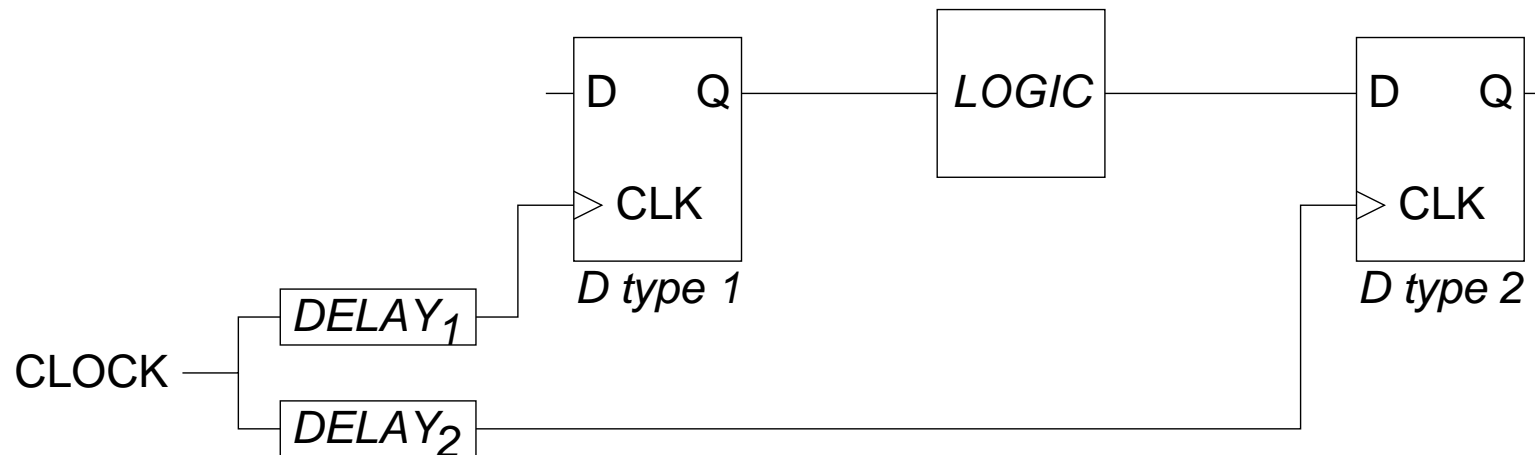

- Hold violation caused by clock skew
  - *D-type 1* clocks first, *D* input of *D-type 2* changes too early  
May occur if difference in clock delays (clock skew) is greater than the delay due to logic and wiring between  $Q_1$  and  $D_2$ .<sup>1</sup>



---

<sup>1</sup>A certain amount of leeway is possible determined by the D-Type characteristics,  $T_q - T_h$

# Clock Distribution

---

- Skew reduction

  


- clock distribution tree
- match all clock paths
- greater clock buffer drive strength will reduce the skew due to imbalance in buffer loadings

# D type Timing

---

- Race hazards with Master Slave D-Types

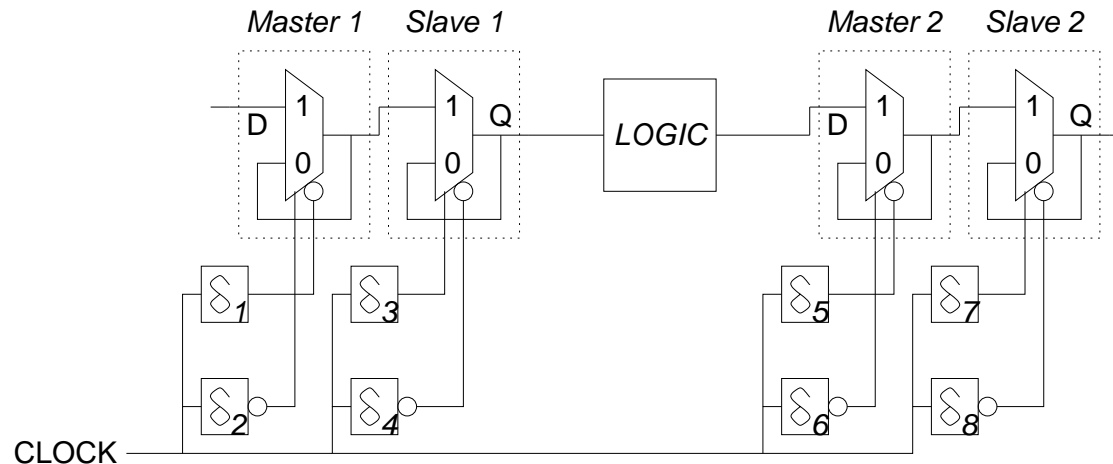


- Rising CLOCK edge  
Delayed latching of *master 2* may leave *slave 1* and *master 2* transparent simultaneously. Data is then transferred in error from *master 1* to *slave 2*.
- Falling CLOCK edge  
Delayed latching of *slave 1* may leave *master 1* and *slave 1* transparent simultaneously.  $Q_1$  will then change in error mid-cycle.
 
# Clock Distribution

---

- Skew reduction for  $clock$  and  $\overline{clock}$ <sup>2</sup>



- minimum load on inverter creating skew
- note  $clock$  and  $\overline{clock}$  signals should be routed together to balance routing delays.


---

<sup>2</sup>we could alternatively generate  $\overline{clock}$  locally within each master slave D Type.

# Clock Distribution

---

- Skew elimination

 


- eliminates skew caused by single inverter
- size transistors to equalize delay
- ensure that load and drive strengths are taken into account

# Clock Distribution

---

- Non-overlapping clocks


 


- guarantees only one latch transparent at any one time

# Clock Distribution

---

- Non-overlapping clocks

  


- clock generation circuit
- this circuit provides clocks which are non-overlapping active high, suitable for use with latches which are transparent with a high clock input.



# D type Timing



- Non-overlapping clocks

 

- inverters provide additional delay to separate phases, may also be the clock buffers
- time between master transparent and slave transparent is wasted
- although we can now cope with large skew it is better to avoid it

# Two Phase Clock Generator (CLKGEN)

---

  

# Non-Inverting Buffer (BUF)

---

