

# Arithmetic - Integer Multiplication

---

- Simple multiplication algorithm.


|                  |   |      |
|------------------|---|------|
| 01010111         | × | 87   |
| 00100101         |   | 37   |
| <hr/>            |   |      |
| 01010111         |   | 609  |
| 00000000         |   | 261  |
| 01010111         |   |      |
| 00000000         |   |      |
| 00000000         |   |      |
| 01010111         |   |      |
| 00000000         |   |      |
| 00000000         |   |      |
| <hr/>            |   |      |
| 0000110010010011 |   | 3219 |

- two  $n$ -bit numbers will produce a  $2n$ -bit result.

# Arithmetic - Integer Multiplication

---

- Implementation

 


– rather slow for single cycle operation

# Arithmetic - Integer Multiplication

---

- Parallel Implementation

 

- should be faster<sup>1</sup>
- faster implementations exist using more complex building blocks


---

<sup>1</sup>note that the overall delay is less than three adder delays due to the skew of rippling carries

# Arithmetic - Integer Multiplication

---

- Multi-cycle implementation

 


- partial product is initially set to zero
- calculation completes after  $n$  cycles (or when  $B = 0$ )

# Arithmetic - Integer Multiplication

---


- Alternative implementation

 

# Arithmetic - Integer Multiplication

---

- Alternative multi-cycle implementation

 


- A is not shifted giving a fixed width value on one input of the adder
- the top  $n-1$  bits of a dedicated adder could be half adders

# Arithmetic - Integer Multiplication

---

- Software implementation

 


- double word result
  - - use multi word shift left and add
- single word result
  - - check for overflow on each addition and each left shift of P

# Arithmetic - Integer Multiplication

---

- Reduce adder widths

 


- each adder produces an  $(n+1)$ -bit result
  - - the least significant bit is fed straight to P
  - - the most significant  $n$  bits are fed to the next adder

# Arithmetic - Integer Multiplication

---

- Multi-cycle implementation

 


- after each addition the least significant bit of the result is placed in P0 which is the least significant word of the partial product

# Arithmetic - Integer Multiplication

---

- Algorithm Comparison

 


- justify each term before addition
- don't justify terms
  - beginning with most significant term add each term to least significant slot and shift left
  - beginning with least significant term add each term to most significant slot and shift right

# Arithmetic - Integer Multiplication

---

- Standard implementation

 

- P0 uses the same register as B
- standard  $n$ -bit adder with carry out

# Arithmetic - Integer Multiplication

---

- Multiplication of 2's complement numbers.


|                  |          |   |       |
|------------------|----------|---|-------|
|                  | 11010111 | × | -41   |
|                  | 00100101 |   | 37    |
| <hr/>            |          |   |       |
| 1111111111010111 |          |   | -287  |
| 0000000000000000 |          |   | -123  |
| 11111111010111   |          |   |       |
| 0000000000000000 |          |   | -1517 |
| 0000000000000000 |          |   |       |
| 11111010111      |          |   |       |
| 000000000000     |          |   |       |
| 000000000000     |          |   |       |
| <hr/>            |          |   |       |
| 1111101000010011 |          |   |       |

- allowing for a negative multiplicand requires only minor modifications (sign extension is used to retain sign information).
- *coping with a negative multiplier is somewhat harder and will not be covered here.*
 
# Arithmetic - Integer Multiplication

---

- Possible implementation?  
signed multiplicand (A) - unsigned multiplier (B)




- we see that we need to perform an arithmetic shift on the result of the addition rather than using the carry out.
- unfortunately this doesn't account for a possible overflow (which will give the wrong sign)
 
# Arithmetic - Integer Multiplication

---

- Standard implementation  
signed multiplicand (A) - unsigned multiplier (B)



- use overflow information to recover the correct sign information (all other bits will be correct when overflow occurs)

## ALU Functionality

---

Where a single cycle multiply is not appropriate we may implement multiply as:

- A multi-cycle instruction
  - The 6809 `MUL` instruction performs a complete multiplication of two unsigned 8-bit numbers yielding a 16-bit result.


$$ACCA' : ACCB' \leftarrow ACCA \times ACCB$$

or

- A single-cycle multiply step instruction
  - The SPARC `MULSCC P1, A, P1` performs a single multiply step instruction. The instruction uses a dedicated `Y` register which contains `B/P0`.

# Arithmetic - Integer Multiplication

- SPARC implementation

 

- takes a step longer due to arrangement of registers and shifters.
- since neither signed nor unsigned numbers are dealt with properly in this system a few additional instructions are used to post-process (fiddle) the answer for signed or unsigned multiplication.