
 


Microprocessor Internals

- Naive view

 


- Linked state machines



Microprocessor Internals


- Datapath

 

- Top Down Design
 - - How many registers?
 - - How many busses?
 - - What data manipulation functions?

Datapath

- Simple Datapath

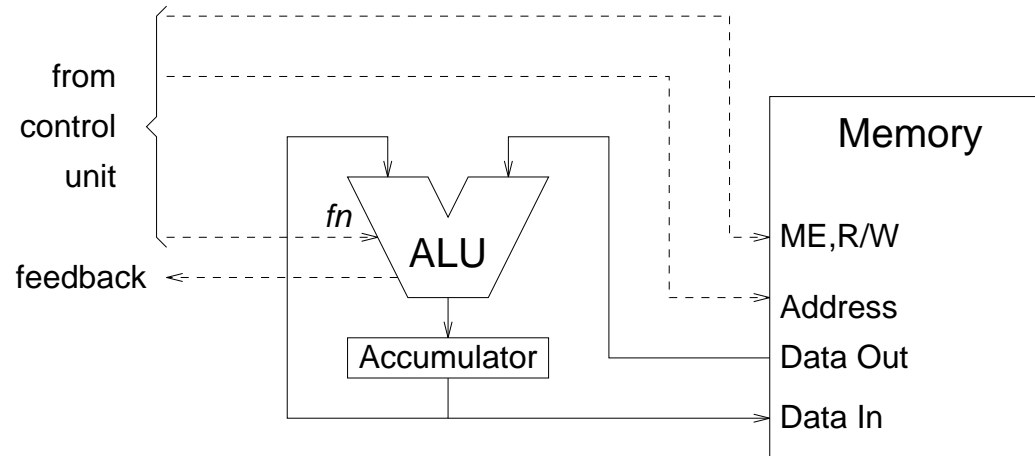

– Register Memory Architecture – Single Address Architecture

Each ALU instruction is of the form;

$$Acc' \leftarrow \mathcal{F}\{Acc, mem(address)\}.$$

Since the accumulator is used as operand and destination, only one address need be specified.

Expression Evaluation

- Consider the HLL statement:

$W := (X + Y) * Z$

- Evaluation:

Instruction	RTL description
-------------	-----------------

LDA x	$Acc' \leftarrow mem(x)$
ADD y	$Acc' \leftarrow Acc + mem(y)$
MUL z	$Acc' \leftarrow Acc \times mem(z)$
STA w	$mem(w)' \leftarrow Acc$

where $W = mem(w)$, $X = mem(x)$, $Y = mem(y)$, $Z = mem(z)$.

i.e. W is a variable stored in the memory at location $w \dots$

ALU Functionality

ALU performs a number of unary and binary arithmetic and logical functions:

- Unary functions

–	A	NOP
–	$\sim A$	COM
–	$A \ll 1$	LSL
–	$A \gg 1$	LSR
–	$-A$	NEG
–	$A + 1$	INC
–	$A - 1$	DEC
–	M	LDA m

ALU Functionality

- Binary functions


- $A \& M$ AND m
- $A | M$ OR m
- $A \wedge M$ EOR m
- $A + M$ ADD m
- $A - M$ SUB m

- Others

- \emptyset CLR

ALU Design

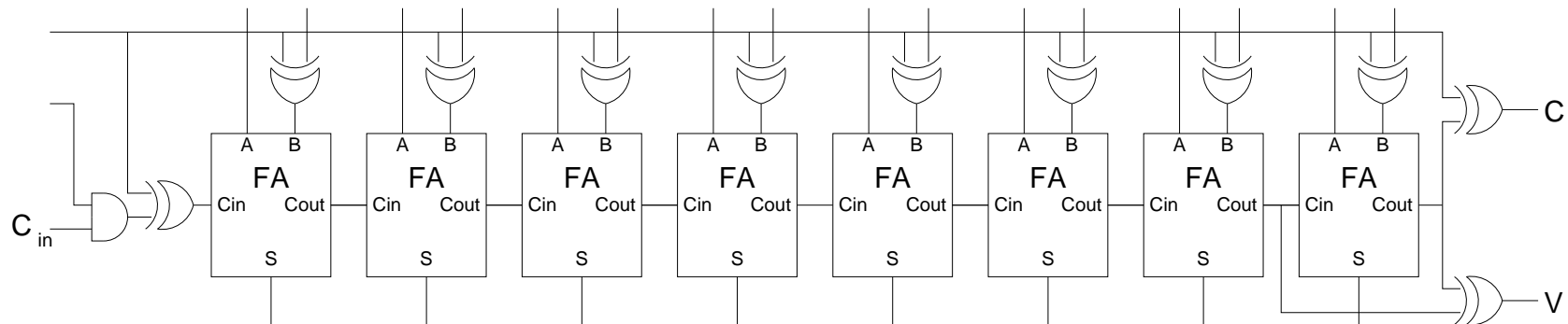
The ALU is designed around the integer adder unit:



A,	NOP,	is implemented as	$\emptyset + A$
$A \ll 1$,	LSL,	is implemented as	$A + A$
-A,	NEG,	is implemented as	$\emptyset - A$
M,	LDA m,	is implemented as	$\emptyset + M$
\emptyset ,	CLR,	is implemented as	$A - A$

ALU Design

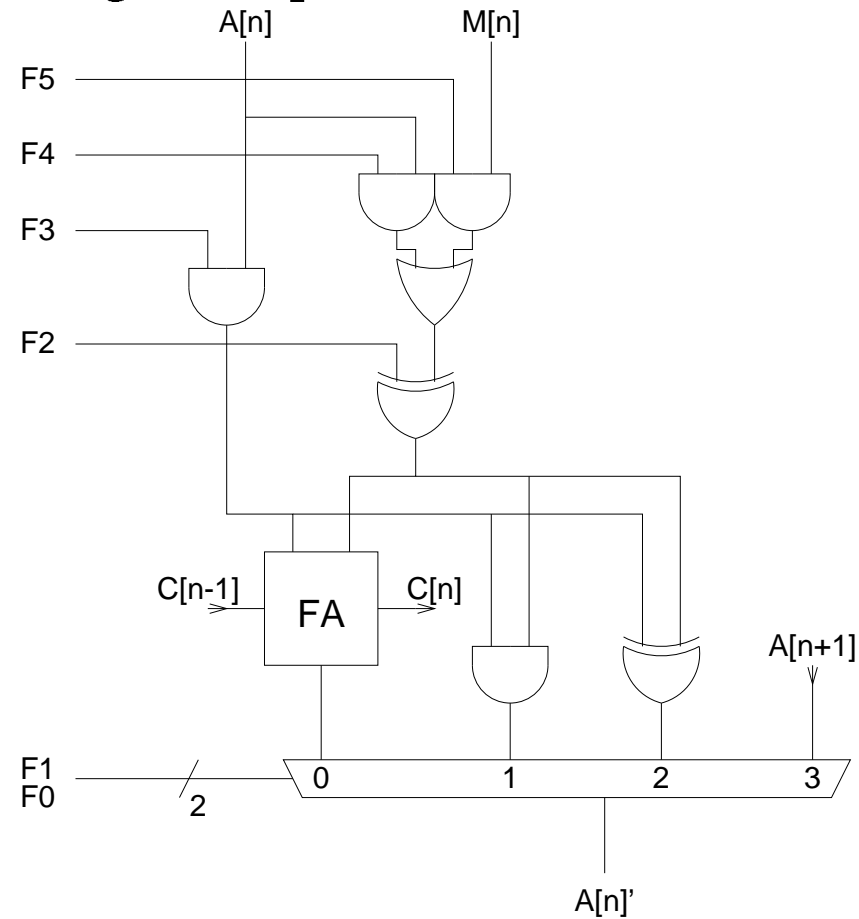A little additional logic completes the ALU functionality¹.



¹note that two of the additional gates may exist within the full adder.

ALU Functionality

- Expensive Functions

The instruction set so far has been based on the arithmetic/logical instructions of the MC6809 processor.

The following functions are expensive in terms of ALU area and have been initially omitted from our design:

- $A * M$ MUL m

requires $n - 1$ n -bit adders for an n -bit multiplication


- $A \ll M$ LSL m

- $A \gg M$ LSR m

require a barrel shifter

ALU Feedback

 - Status Flags exist to retain overflow information between arithmetic operations:



- the latched overflow information is fed back to the controller.
- the flags are only updated when an arithmetic operation is performed.

Multi-word Arithmetic

- The carry out overflow flag can be used to support multi-word signed and unsigned arithmetic:

Evaluation of $Z := X + Y$ for double-word addition²:



LDA <i>x_lo</i>	$Acc' \leftarrow mem(x_lo)$
ADD <i>y_lo</i>	$\{C' : Acc'\} \leftarrow Acc + mem(y_lo)$
STA <i>z_lo</i>	$mem(z_lo)' \leftarrow Acc$
LDA <i>x_hi</i>	$Acc' \leftarrow mem(x_hi)$
ADC <i>y_hi</i>	$\{C' : Acc'\} \leftarrow Acc + mem(y_hi) + C$
STA <i>z_hi</i>	$mem(z_hi)' \leftarrow Acc$

- after the ADD instruction the intermediate carry is stored in *C*.
- for the ADC instruction the ALU is configured such that *C* is used for carry in and carry out.

²use SUB and SBC for subtraction

Multi-word Arithmetic


- Multi-word logical shifts:

  

- LDA x_hi; LSR; STA x_hi; LDA x_lo; ROR; STA x_lo;
performs double word shift right.
- LDA x_lo; LSL; STA x_lo; LDA x_hi; ROL; STA x_hi;
performs double word shift left.

More Shifts

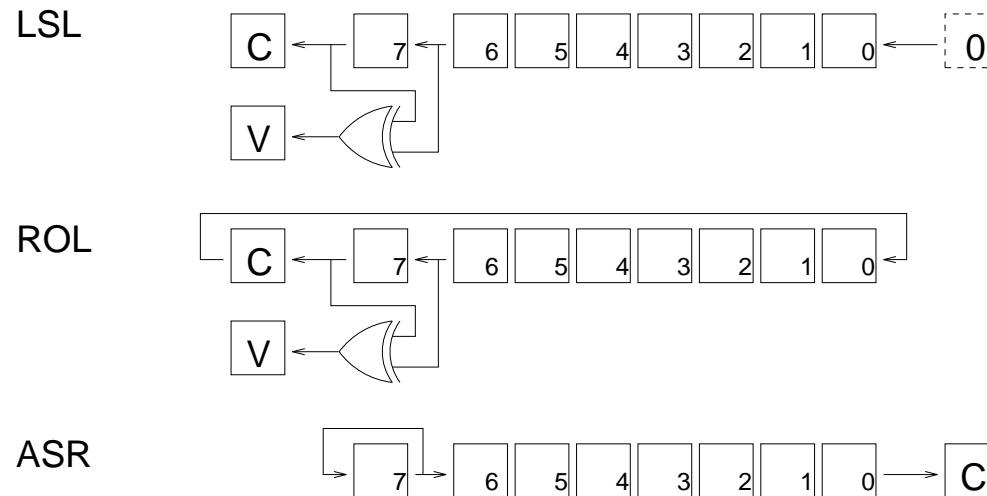- Shifts of signed numbers (arithmetic shifts):




- LSL and ROL are used for multiplication by 2. These instructions must set V in the case of a signed arithmetic overflow.
- A special instruction ASR^3 performs divide by 2 for signed numbers.

³LSL is also known as ASL

ALU Feedback

Other signals, N and Z , are fed back to the controller to indicate whether a result is negative or zero.

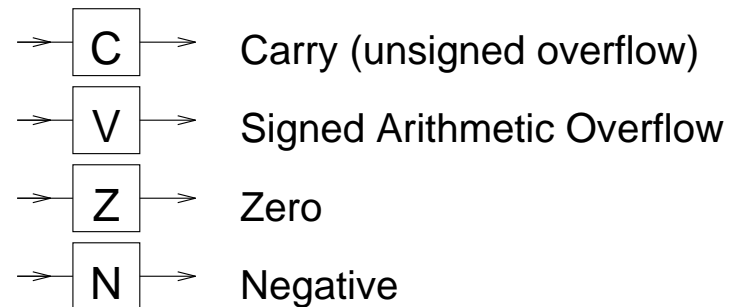These signals may be taken directly from the accumulator or they may be latched, like C and V , only on appropriate instructions⁴.



The four feedback signals are used to control the program flow.

⁴flags are usually latched for processors with more than one data register