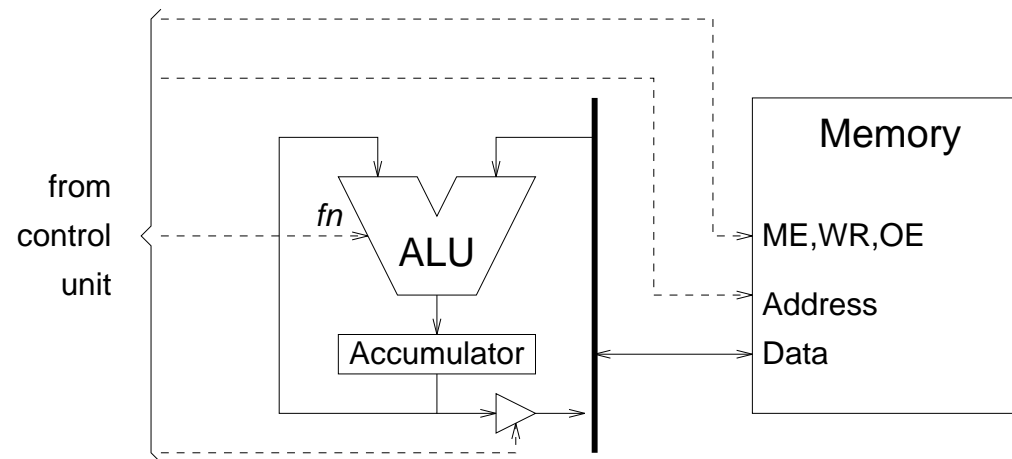


# Datapath

---

- Bus Based Architecture




Since wiring on a chip is expensive (requires a lot of area) we wish to limit the number of busses which need to be routed. A single data bus will be used wherever possible.

# Microprocessor

---

- Including Control Unit

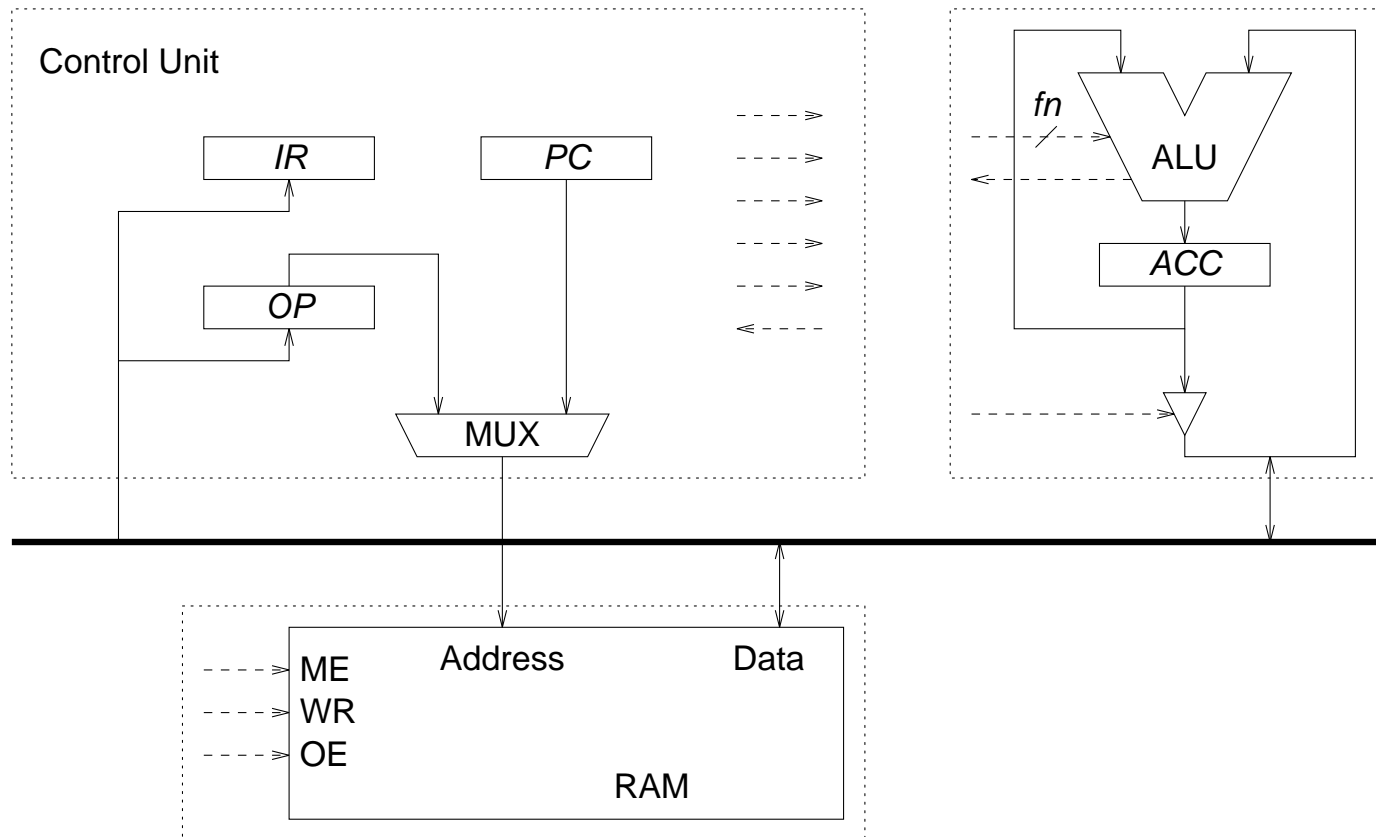

# Microprocessor

---

- Instruction Cycle

- ALU operation

1	$IR' \leftarrow mem(PC)$	$PC' \leftarrow PC + 1$
2	$OP' \leftarrow mem(PC)$	$PC' \leftarrow PC + 1$
3	$Acc' \leftarrow \mathcal{F}\{Acc, mem(OP)\}$	

Each stage includes one memory access.

- For synchronous single cycle memory<sup>1</sup>, the complete instruction cycle takes 3 clock cycles.
- For multi cycle memory we may expect the instruction cycle to take 9 or more cycles.

Each memory access will include address setup, data access & data hold cycles.

---


<sup>1</sup>i.e.  $ME = \overline{CLK}$

# Microprocessor

---

Faster access is possible where the instruction register is large enough to include operand information as well as instruction information.

- Modified Control Unit

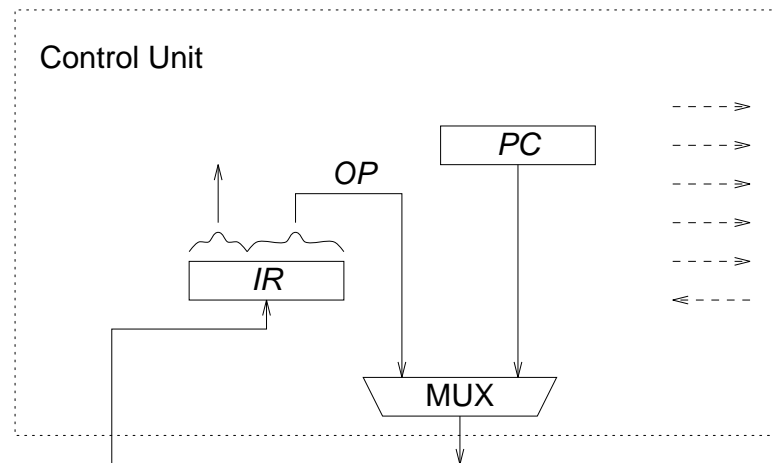

# Microprocessor

---

- Instruction Cycles

- ALU operation

1	$IR' \leftarrow mem(PC)$	$PC' \leftarrow PC + 1$
2	$Acc' \leftarrow \mathcal{F}\{Acc, mem(OP)\}$	

- Store Operation

1	$IR' \leftarrow mem(PC)$	$PC' \leftarrow PC + 1$
2	$mem(OP)' \leftarrow Acc$	

- Branch Operation

- - taken

1	$IR' \leftarrow mem(PC)$	$PC' \leftarrow PC + 1$
2	$PC' \leftarrow PC + OP$	

- - not taken


1	$IR' \leftarrow mem(PC)$	$PC' \leftarrow PC + 1$
---	--------------------------	-------------------------

# Microprocessor

---

- Program Counter Unit

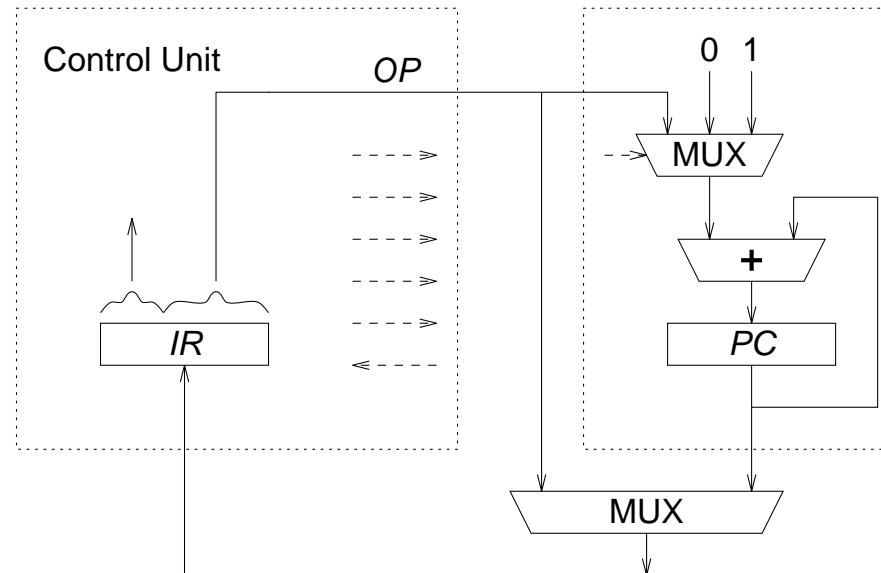We can continue our top down approach by completing the design of a program counter unit:




In each cycle we add 0 or 1 or  $OP$  to the  $PC$ .

# Microprocessor

---

- Complete Architecture

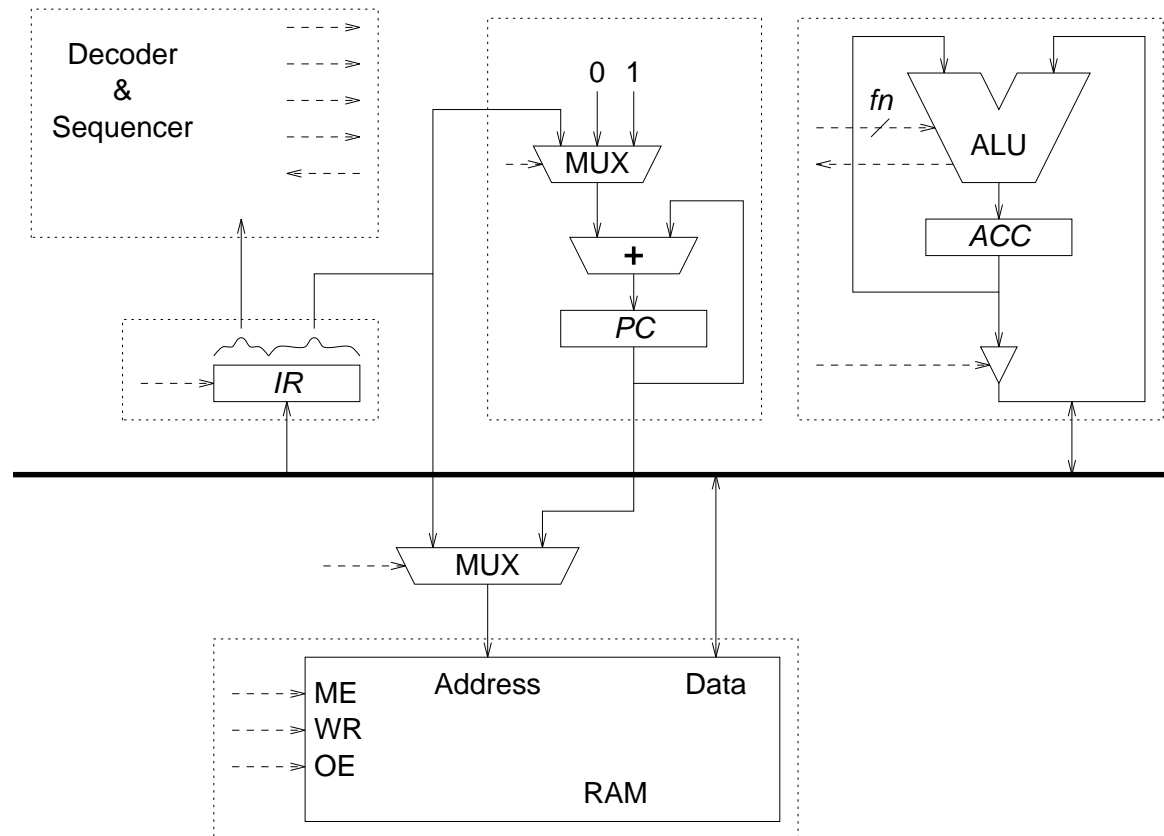

# Microprocessor

---


- Complete Architecture
  - Well defined functional blocks
    - - Distinct Functionality
    - - Minimum Data Transfer
  - Simple Decoder & Sequencer
    - - Well Defined Instruction Cycles
    - - Simple Control
    - - Simple Feedback



# Microprocessor

---

- Single Bus Architecture

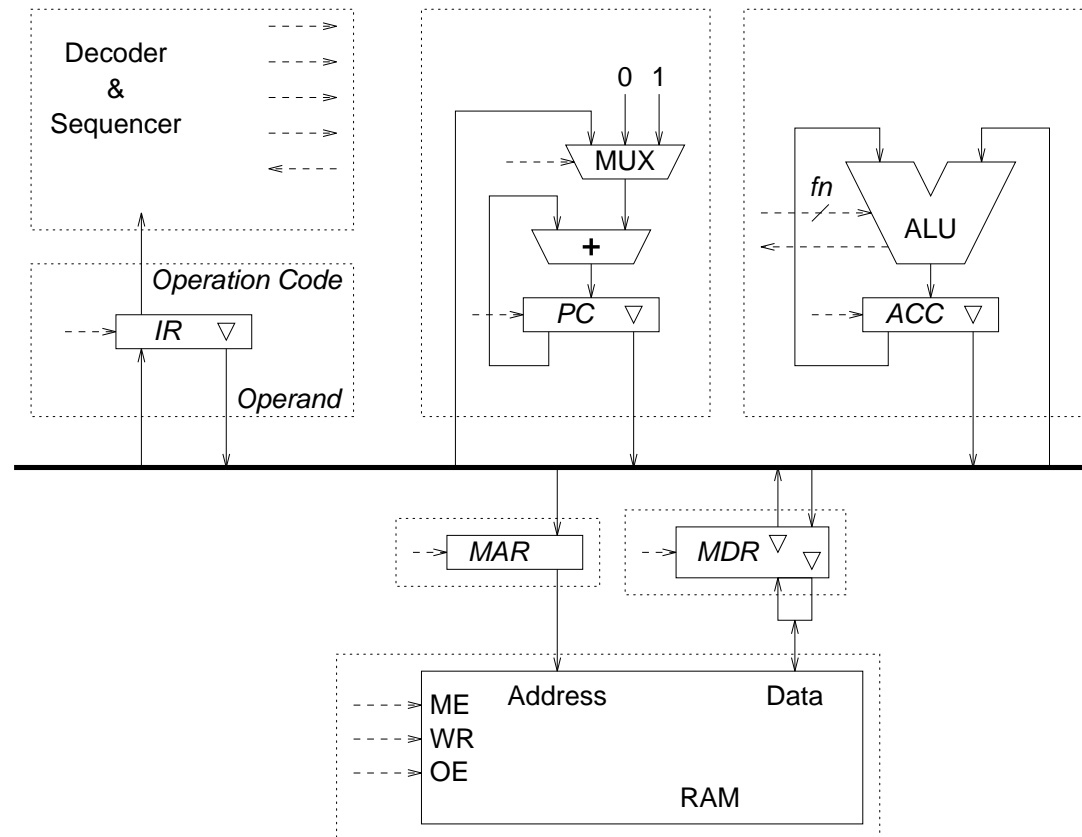

# Microprocessor

---

## Addressing Modes

- Direct Addressing

Operand field contains the address of the data for manipulation

ADD *addr*

$$Acc' \leftarrow Acc + mem(addr)$$

The use of a single bus architecture opens up the possibility of other addressing modes.

# Microprocessor

---

## Addressing Modes

- Immediate Addressing

Operand field contains the data for manipulation

ADD #num                       $Acc' \leftarrow Acc + num$

- Indirect Addressing

Operand field contains the address of a pointer to the data for manipulation

ADD (point\_addr)       $Acc' \leftarrow Acc + mem(mem(point\_addr))$

# Instruction Cycle

---

- Instruction Fetch

$$1 \quad MAR' \leftarrow PC \qquad PC' \leftarrow PC + 1$$

$$2 \quad MDR' \leftarrow mem(MAR)$$

$$3 \quad IR' \leftarrow MDR$$

- Bus Allocation

- - During each clock cycle only one source may drive the bus.
    - - The bus is driven by  $PC$  in cycle 1 and by  $MDR$  in cycle 3.
    - - Cycle 2 is a memory access cycle; here the bus is unused.

- Instruction Execute

The number of cycles and the action to be taken in each cycle are dependent on the type of instruction and the addressing mode.

# Instruction Cycle

---

- ALU instructions

Inherent	COM		$ACC' \leftarrow \sim ACC$
Immediate	AND	#n	$ACC' \leftarrow ACC \& OP$
Direct	XOR	m	$MAR' \leftarrow OP$
			$MDR' \leftarrow mem(MAR)$
			$ACC' \leftarrow ACC \wedge MDR$
Indirect	OR	(p)	$MAR' \leftarrow OP$
			$MDR' \leftarrow mem(MAR)$
			$MAR' \leftarrow MDR$
			$MDR' \leftarrow mem(MAR)$
			$ACC' \leftarrow ACC \mid MDR$

# Instruction Cycle

---

- Store Instructions

Direct	STA m	$MAR' \leftarrow OP$ $MDR' \leftarrow ACC$ $mem(MAR)' \leftarrow MDR$
Indirect	STA (p)	$MAR' \leftarrow OP$ $MDR' \leftarrow mem(MAR)$ $MAR' \leftarrow MDR$ $MDR' \leftarrow ACC$ $mem(MAR)' \leftarrow MDR$

- Branch Instructions

Unconditional	BRA m	$PC' \leftarrow PC + OP$
Conditional	BCS m	$IF (C=1) THEN PC' \leftarrow PC + OP$

# Microprocessor

---

- Indexed Addressing

Addresses are relative to an index register

ADDA  $X, n$

$$Acc' \leftarrow Acc + mem(X + n)$$

- additional registers<sup>2</sup>
- address calculation
  - - dedicated address generation unit?
  - - in ALU?


---

<sup>2</sup>note that we now have to specify the accumulator A for addition to avoid ambiguity.
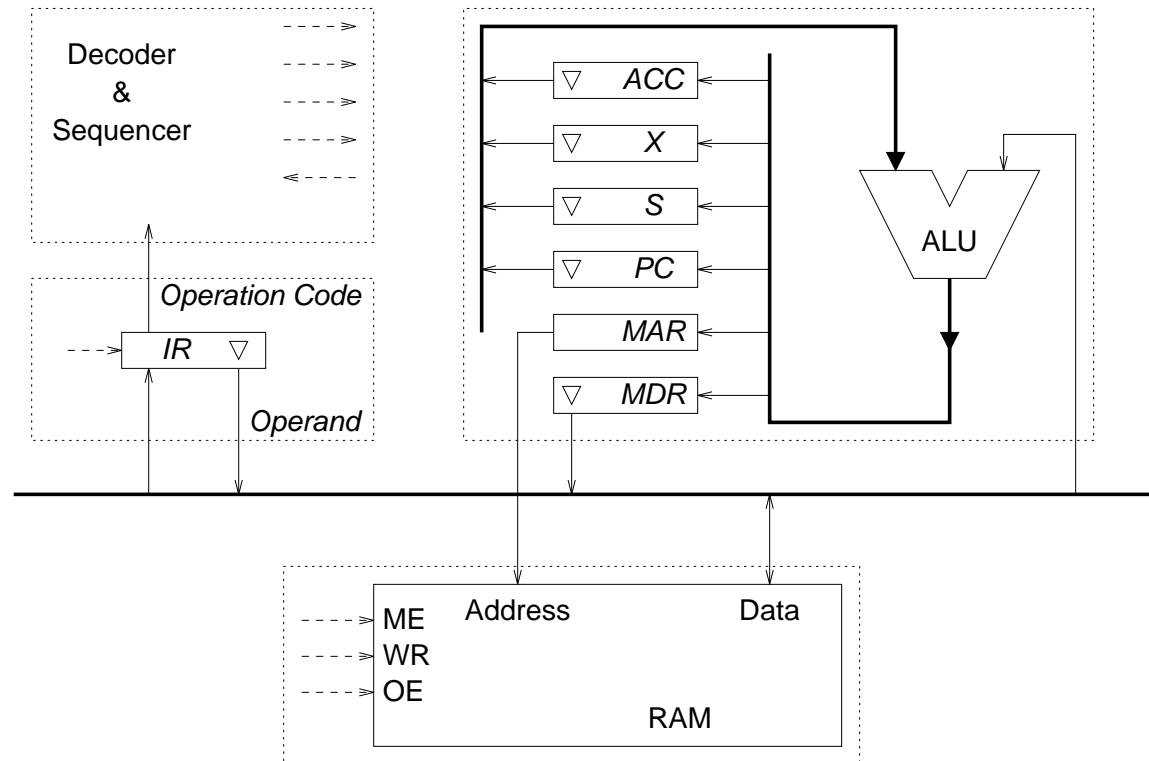
# Microprocessor

---

- Multiple Special Purpose Registers
- Three Busses





# Microprocessor

---

ALU is shared:

- Program Counter

$$PC' \leftarrow MAR' \leftarrow PC + 1$$


- Address Generation

$$MAR' \leftarrow \mathcal{F}\{X, ?\}$$

- Arithmetic Logic

$$Acc' \leftarrow \mathcal{F}\{Acc, ?\}$$

 The results is a reduction in cost with a possible time penalty, various enhancements may be employed to reduce the number of cycles:



# Microprocessor

---

- More addressing modes

- Stack (Push & Pull)

STA  $-S$

$$S' \leftarrow S - 1$$

$$mem(S)' \leftarrow Acc$$

ADDA  $S+$

$$Acc' \leftarrow Acc + mem(S)$$

$$S' \leftarrow S + 1$$

- (Pre-)Indexed Indirect


ADDA  $(X, n)$

$$Acc' \leftarrow Acc + mem(mem(X + n))$$
 
# Microprocessor

---

- General Purpose Registers
- Register Register Architectures – Three Address Architecture




Each ALU instruction is of the form;

$$R[z]' \leftarrow \mathcal{F}\{R[x], R[y]\}.$$

# Microprocessor

---

- Immediate Data

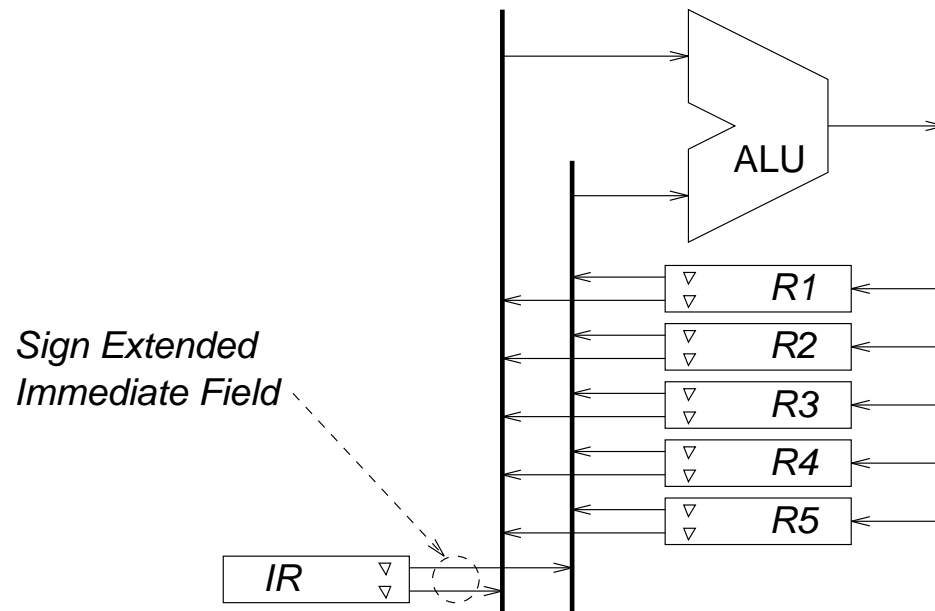


This implementation allows immediate addressing for ALU instructions;

$$R[z]' \leftarrow \mathcal{F}\{R[x], imm\}.$$

# Microprocessor

---

- Memory Access

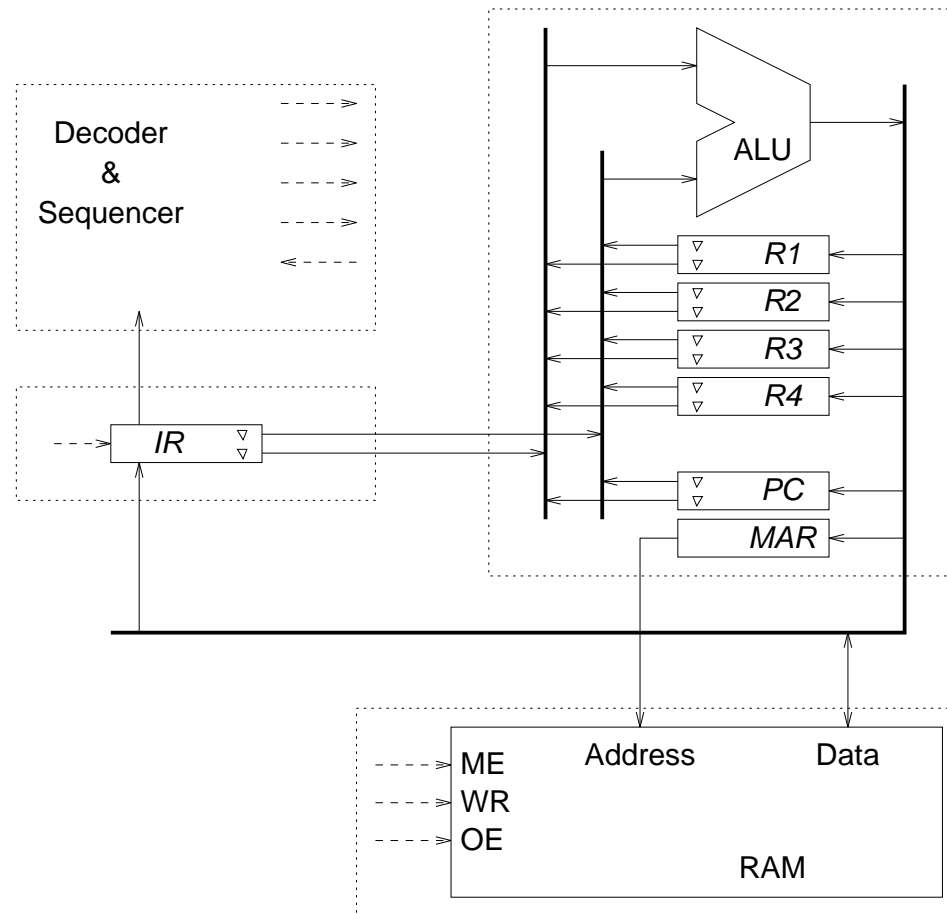

# Microprocessor

---

- Memory Access

Memory access is accomplished in two stages

- Address generation

$$MAR' \leftarrow \mathcal{F}\{R[x], R[y]\}$$

- Data Access

- - Read

$$R[z]' \leftarrow mem(MAR)$$

- - Write<sup>3</sup>

$$mem(MAR)' \leftarrow R[z]$$

---

<sup>3</sup>note that during memory write data is fed unmodified through the ALU.

# Microprocessor

---

- Memory Access

Given the larger number of general purpose registers we need fewer addressing modes for load & store operations:

$$MAR' \leftarrow imm$$

or

$$MAR' \leftarrow R[x]$$

or

$$MAR' \leftarrow R[x] + imm$$

or

$$MAR' \leftarrow R[x] + R[y].$$

# Microprocessor

---

Control transfer instructions may be PC relative or register indirect.

- PC relative

$$PC' \leftarrow PC + imm$$

- Register indirect

$$PC' \leftarrow R[x]$$

Since the latter is not limited to a sign extended offset the transfer can be to any location in memory.

Any of our general purpose registers may contain data, data address or program address.