
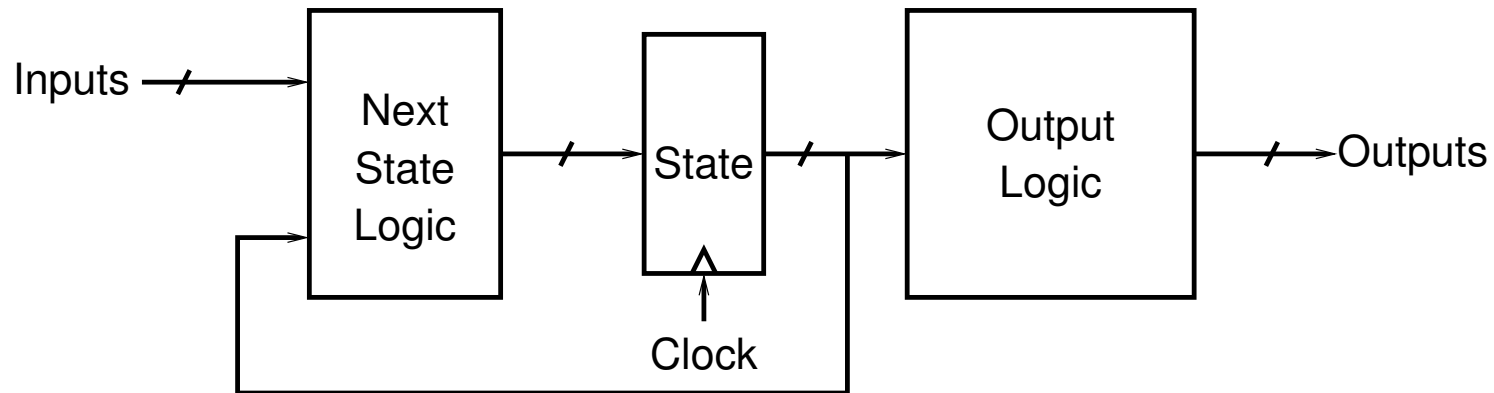


ASM


Moore State Machine

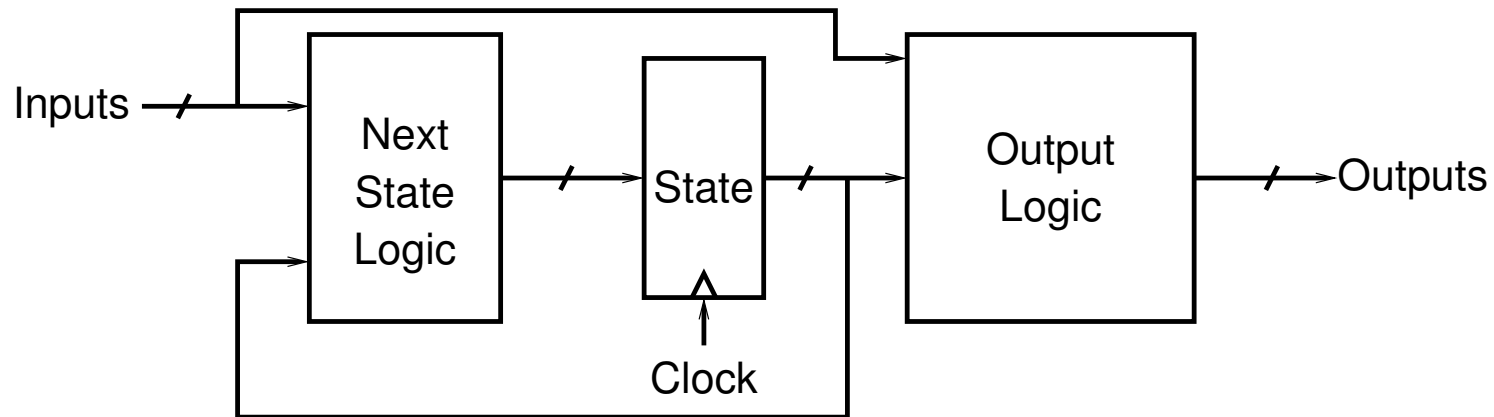


Mealy State Machine




ASM1 – Moore Machine

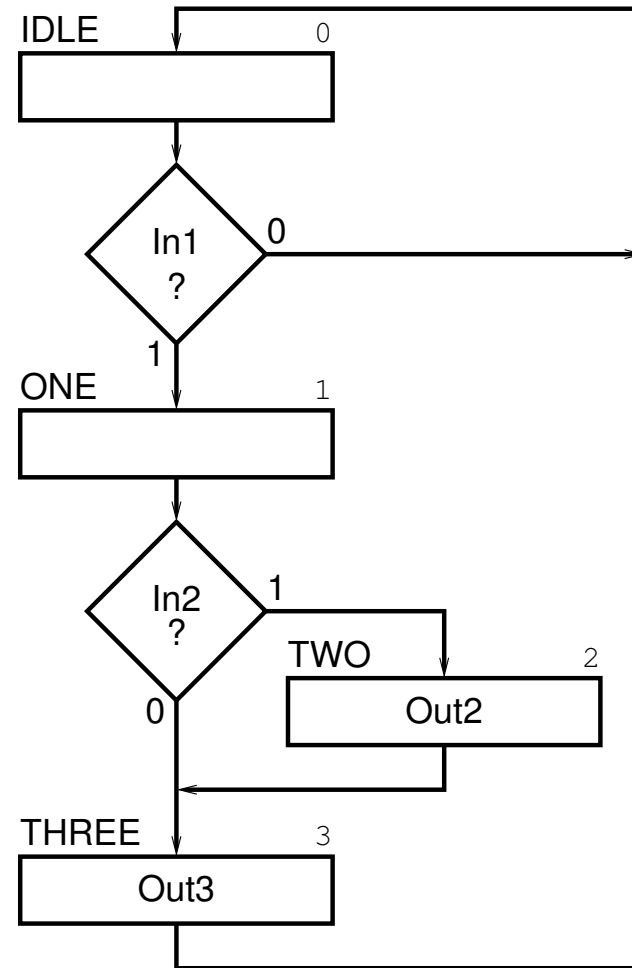

ASM1 – Moore Machine

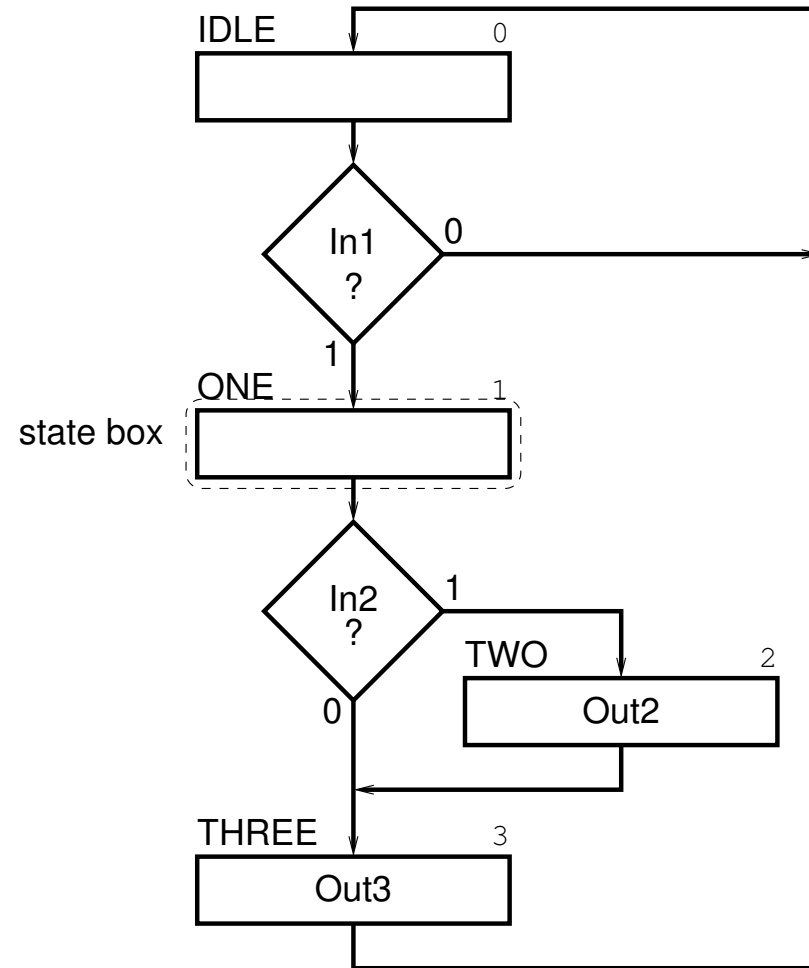


ASM1 – Moore Machine

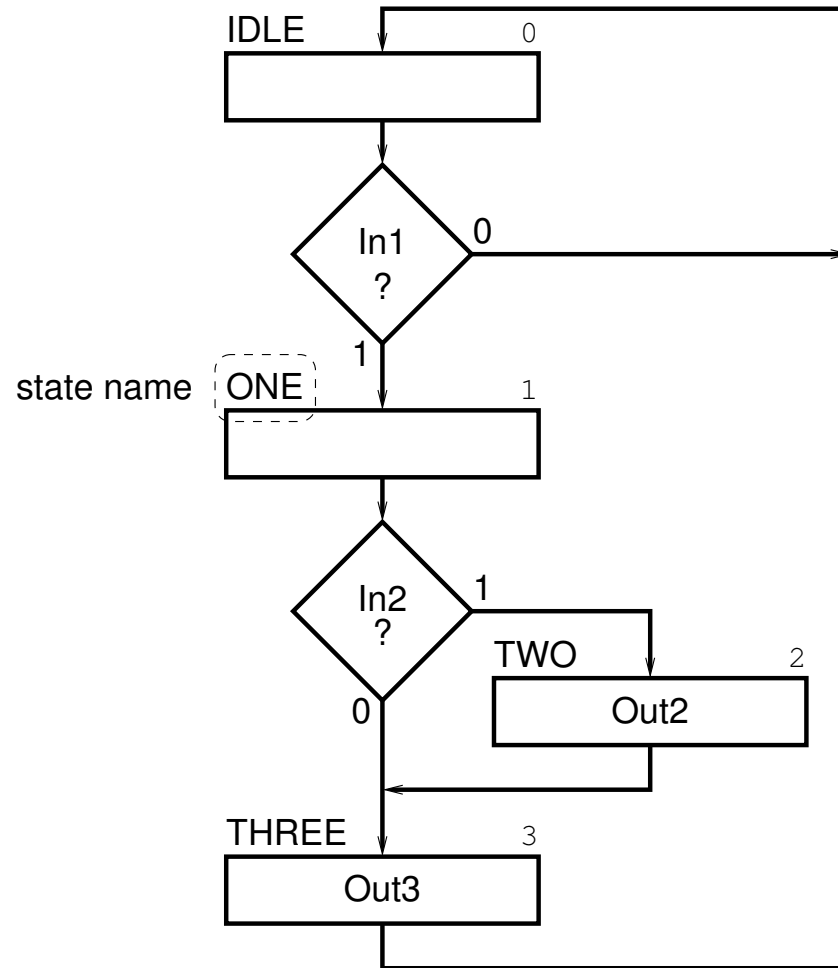





ASM1 – Moore Machine

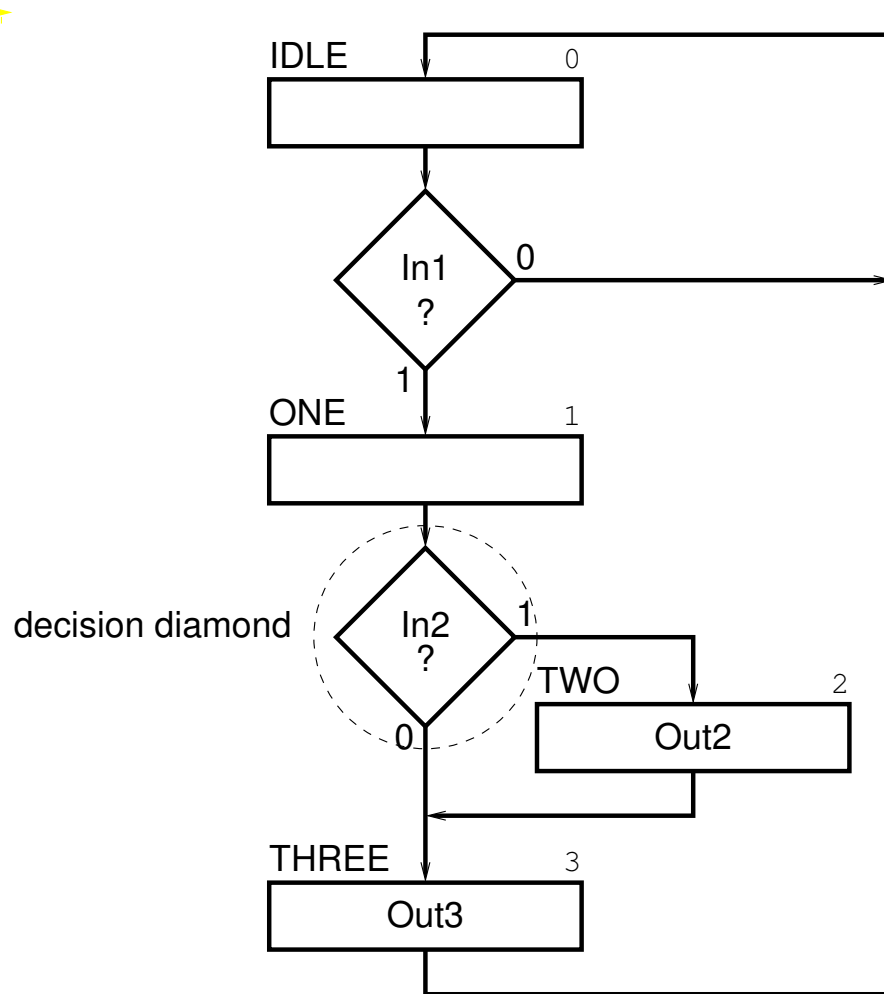

ASM1 – Moore Machine

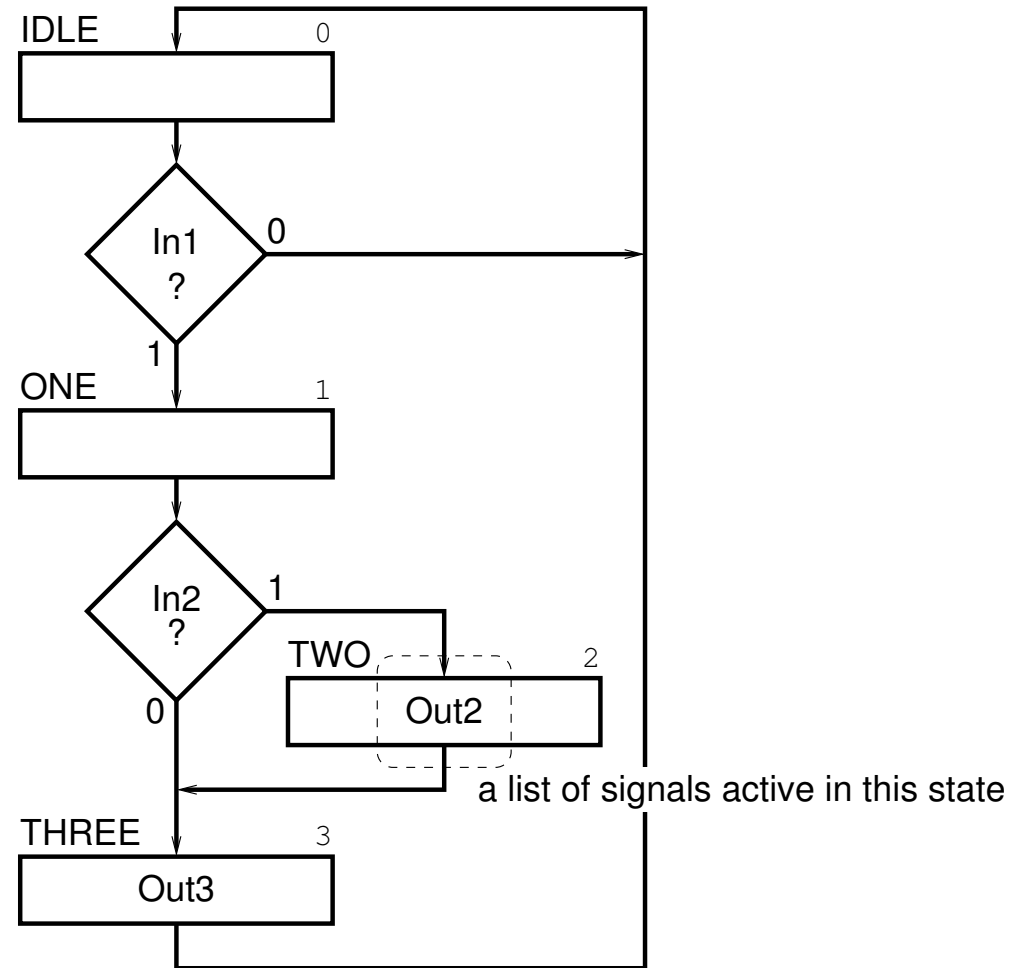

ASM1 – Moore Machine

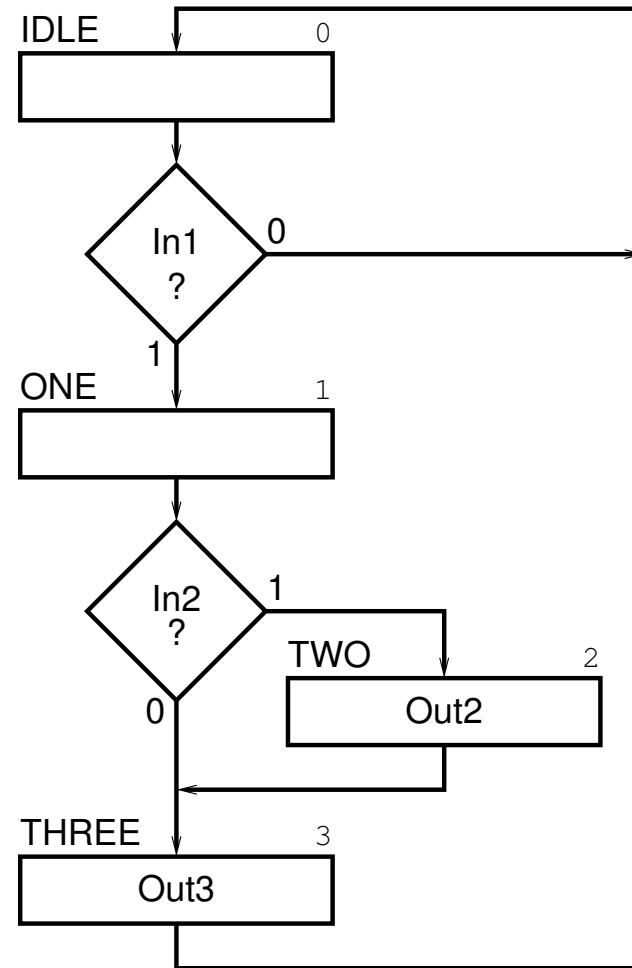

ASM1^a

```
// ----- state declaration -----  
logic [1:0] state;  
  
// ----- state + next state logic -----  
always_ff @(posedge Clock, negedge nReset)  
    if (!nReset)          state <= 0;  
    else  
        case (state)  
            0:          if (In1)  state <= 1;  
            1:          if (In2)  state <= 2;  
                   else          state <= 3;  
            2:          state <= 3;  
            3:          state <= 0;  
        endcase  
  
// ----- output logic -----  
logic Out2, Out3;  
    assign Out2 = (state == 2);  
    assign Out3 = (state == 3);
```

ASM1^b – using state names and **enumerated** types¹

```
// ----- state declaration -----  
enum logic [1:0] { IDLE=0, ONE=1, TWO=2, THREE=3 } state;  
  
// ----- state + next state logic -----  
always_ff @(posedge Clock, negedge nReset)  
    if (!nReset)          state <= IDLE;  
    else  
        case (state)  
            IDLE : if (In1)  state <= ONE;  
            ONE  : if (In2)  state <= TWO;  
                   else      state <= THREE;  
            TWO  :          state <= THREE;  
            THREE:          state <= IDLE;  
        endcase  
  
// ----- output logic -----  
logic Out2, Out3;  
    assign Out2 = (state == TWO);  
    assign Out3 = (state == THREE);
```

¹a synthesis program may re-allocate the states
(the default state assignments shown here are optional)

ASM1^b – using state names and **enumerated** types¹

```
// ----- state declaration -----  
enum logic [1:0] { IDLE , ONE , TWO , THREE } state;  
  
// ----- state + next state logic -----  
always_ff @(posedge Clock, negedge nReset)  
    if (!nReset)          state <= IDLE;  
    else  
        case (state)  
            IDLE : if (In1) state <= ONE;  
            ONE  : if (In2) state <= TWO;  
                   else      state <= THREE;  
            TWO  :          state <= THREE;  
            THREE:          state <= IDLE;  
        endcase  
  
// ----- output logic -----  
logic Out2, Out3;  
    assign Out2 = (state == TWO);  
    assign Out3 = (state == THREE);
```

¹a synthesis program may re-allocate the states
(the default state assignments shown here are optional)

ASM1^b – using state names and **enumerated** types²

```
// ----- state declaration -----  
enum logic [1:0] { IDLE=0, ONE=1, TWO=2, THREE=3 } state;  
  
// ----- state + next state logic -----  
always_ff @(posedge Clock, negedge nReset)  
  if (!nReset)          state <= IDLE;  
  else  
    case (state)  
      IDLE : if (In1)  state <= ONE;  
      ONE  : if (In2)  state <= TWO;  
              else    state <= THREE;  
      TWO  :          state <= THREE;  
      THREE:          state <= IDLE;  
    endcase  
  
// ----- output logic -----  
logic Out2, Out3;  
  assign Out2 = (state == TWO);  
  assign Out3 = (state == THREE);
```

²a synthesis program may re-allocate the states
(the default state assignments shown here are optional)

ASM1^c – using a procedural block to infer combinational logic

```
// ----- state declaration -----  
enum logic [1:0] { IDLE, ONE, TWO, THREE } state;  
  
// ----- state + next state logic -----  
always_ff @(posedge Clock, negedge nReset)  
    if (!nReset)          state <= IDLE;  
    else  
        case (state)  
            IDLE : if (In1)  state <= ONE;  
            ONE  : if (In2)  state <= TWO;  
                   else      state <= THREE;  
            TWO  :          state <= THREE;  
            THREE:          state <= IDLE;  
        endcase  
  
// ----- output logic -----  
logic Out2, Out3;  
always_comb  
    begin  
        Out2 = (state == TWO);  
        Out3 = (state == THREE);  
    end
```

ASM1^d – using typedef

```
// ----- state declaration -----
typedef enum logic [1:0] { IDLE, ONE, TWO, THREE } state_t;
state_t state;
// ----- state + next state logic -----
always_ff @(posedge Clock, negedge nReset)
    if (!nReset)          state <= IDLE;
    else
        case (state)
            IDLE : if (In1)  state <= ONE;
            ONE  : if (In2)  state <= TWO;
                   else      state <= THREE;
            TWO  :           state <= THREE;
            THREE:           state <= IDLE;
        endcase

// ----- output logic -----
logic Out2, Out3;
always_comb
    begin
        Out2 = (state == TWO);
        Out3 = (state == THREE);
    end
```

ASM1^e – using **if else** instead of **case**

```
// ----- state declaration -----  
enum logic [1:0] { IDLE, ONE, TWO, THREE } state;  
  
// ----- state + next state logic -----  
always_ff @(posedge Clock, negedge nReset)  
    if (!nReset)          state <= IDLE;  
    else  
        if ((state == IDLE) && In1)  
            state <= ONE;  
        else if ((state == ONE) && In2)  
            state <= TWO;  
        else if ((state == ONE) || (state == TWO))  
            state <= THREE;  
        else  
            state <= IDLE;  
// ----- output logic -----  
logic Out2, Out3;  
always_comb  
    begin  
        Out2 = (state == TWO);  
        Out3 = (state == THREE);  
    end
```

ASM1^f – multiple assignment (default and override)

```
// ----- state declaration -----
enum logic [1:0] { IDLE, ONE, TWO, THREE } state;

// ----- state + next state logic -----
always_ff @(posedge Clock, negedge nReset)
    if (!nReset)          state <= IDLE;
    else
        case (state)
            IDLE : if (In1)  state <= ONE;
            ONE  : if (In2)  state <= TWO;
                   else      state <= THREE;
            TWO  :           state <= THREE;
            THREE:           state <= IDLE;
        endcase

// ----- output logic -----
logic Out2, Out3;
always_comb
    begin
        Out2 = 0; Out3 = 0;           // <- default values assigned here

        if ( state == TWO )    Out2 = 1; // <- only non-default values
        if ( state == THREE ) Out3 = 1; //      assigned here
    end
```

ASM1^g – multiple assignment (default and override) with **case**

```
// ----- state declaration -----  
enum logic [1:0] { IDLE, ONE, TWO, THREE } state;  
  
// ----- state + next state logic -----  
always_ff @(posedge Clock, negedge nReset)  
    if (!nReset)          state <= IDLE;  
    else  
        case (state)  
            IDLE : if (In1)  state <= ONE;  
            ONE  : if (In2)  state <= TWO;  
                   else      state <= THREE;  
            TWO  :          state <= THREE;  
            THREE:          state <= IDLE;  
        endcase  
  
// ----- output logic -----  
logic Out2, Out3;  
always_comb  
    begin  
        Out2 = 0; Out3 = 0;          // <- default values assigned here  
        case (state)  TWO   : Out2 = 1; // <- only non-default values  
                       THREE : Out3 = 1; //      assigned here  
        endcase  
    end
```

ASM1^h – using a single procedural block *(This style is not advised for novices!)*³

// Caution: infers registered outputs for Out2 and Out3

```
enum logic [1:0] { IDLE, ONE, TWO, THREE } state;
logic Out2, Out3;

always_ff @(posedge Clock, negedge nReset)
    if (!nReset)          begin state <= IDLE;
                           Out2  <= 0; Out3 <= 0; end
    else
        begin
            Out2 <= (state == ONE) && In2;
            Out3 <= (state == ONE) && !In2 || (state == TWO);
            case (state)
                IDLE : if (In1)      state <= ONE;
                ONE  : if (In2)      state <= TWO;
                       else        state <= THREE;
                TWO  :              state <= THREE;
                THREE:              state <= IDLE;
            endcase
        end
end
```

³here we predict in one state, the outputs that we need in the next state
– it is hard to see which output is associated with which state ∴ error prone

ASM1ⁱ – using a single procedural block *(This style is not advised for novices!)*⁴

// Caution: infers registered outputs for Out2 and Out3

```
enum logic [1:0] { IDLE, ONE, TWO, THREE } state;
logic Out2, Out3;

always_ff @(posedge Clock, negedge nReset)
  if (!nReset) begin state <= IDLE;
                Out2 <= 0; Out3 <= 0; end

  else
    case (state)
      IDLE : if (In1) begin state <= ONE;
                Out2 <= 0; Out3 <= 0; end

      ONE  : if (In2) begin state <= TWO;
                Out2 <= 1; Out3 <= 0; end

                else begin state <= THREE;
                Out2 <= 0; Out3 <= 1; end

      TWO  : begin state <= THREE;
                Out2 <= 0; Out3 <= 1; end

      THREE: begin state <= IDLE;
                Out2 <= 0; Out3 <= 0; end

    endcase
```

⁴here the outputs are clearly associated with the appropriate states
– includes duplicated sections of code ∴ error prone

ASM1^j – using a single procedural block *(This style is not advised for novices!)*⁵

// Caution: infers registered outputs for Out2 and Out3

```
enum logic [1:0] { IDLE, ONE, TWO, THREE } state;
logic Out2, Out3;


always_ff @(posedge Clock, negedge nReset)
  if (!nReset) begin state <= IDLE;
                                Out2 <= 0; Out3 <= 0; end

  else
    if ((state == IDLE) && In1)
      begin state <= ONE;
                                Out2 <= 0; Out3 <= 0; end
    else if ((state == ONE) && In2)
      begin state <= TWO;
                                Out2 <= 1; Out3 <= 0; end
    else if ((state == ONE) || (state == TWO))
      begin state <= THREE;
                                Out2 <= 0; Out3 <= 1; end
    else
      begin state <= IDLE;
                                Out2 <= 0; Out3 <= 0; end
```

⁵here **if else** structure is used to avoid duplication of state THREE code
– the resulting code is not easy to follow ∴ error prone

ASM1* – Moore Machine

(with optimized state coding)

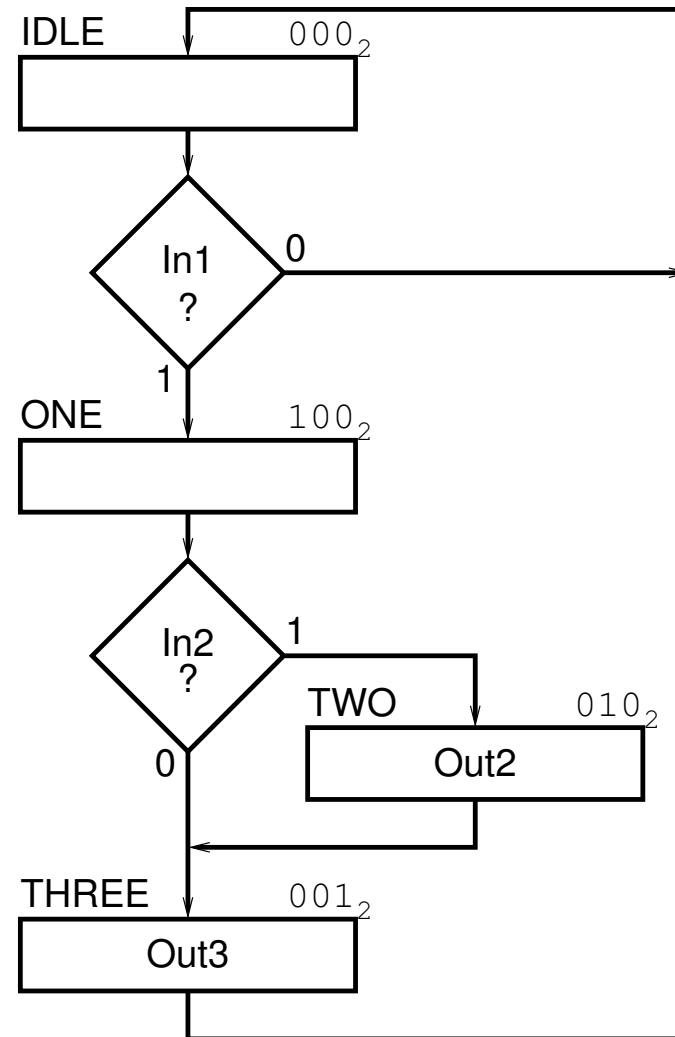

ASM1^k – using a single procedural block

(with optimized state coding)⁶

```
typedef enum logic [2:0]
{ IDLE=3'b000, ONE=3'b100, TWO=3'b010, THREE=3'b001 } state_t;
logic state, Out2, Out3;

always_ff @(posedge Clock, negedge nReset)
  if (!nReset) {state,Out2,Out3} <= IDLE;
  else
    case ({state,Out2,Out3})
      IDLE : if (In1) {state,Out2,Out3} <= ONE;
             else    {state,Out2,Out3} <= IDLE;
      ONE  : if (In2) {state,Out2,Out3} <= TWO;
             else    {state,Out2,Out3} <= THREE;
      TWO  :          {state,Out2,Out3} <= THREE;
      THREE:          {state,Out2,Out3} <= IDLE;
    endcase
```

⁶here the outputs are considered to be part of the state

- **typedef** is used to define `state_t` but `state_t` is never used
 - only the state names are used
 - `state` is a single bit logic variable
- the resulting code is concise but is it easy to follow?


ASM - Single Procedural Block Approach?

Some ASMs lend themselves to implementation as a single procedural block ...

State + Next State Logic	Output Logic	
always_ff	assign	✓
always_ff	always_comb	✓
always_ff		✓

ASM - Single Procedural Block Approach?

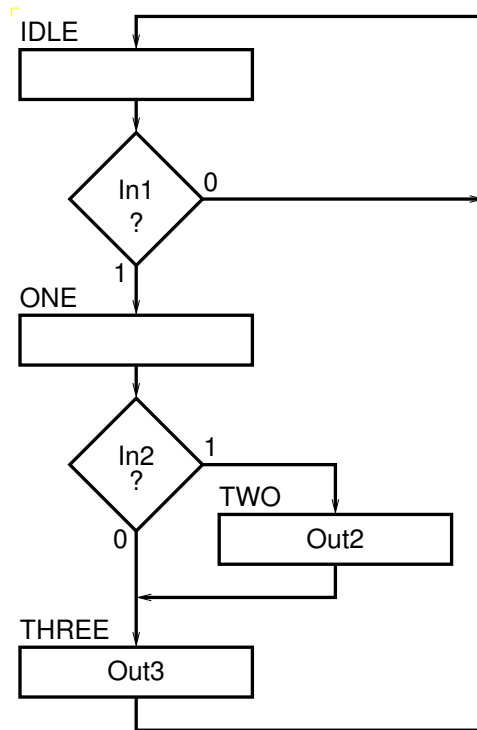
Some ASMs lend themselves to implementation as a single procedural block ...




State + Next State Logic	Output Logic	
<code>always_ff</code>	<code>assign</code>	✓
<code>always_ff</code>	<code>always_comb</code>	✓
<code>always_ff</code>		✗

This is **NOT** one of them.


ASM2 – Mealy Machine

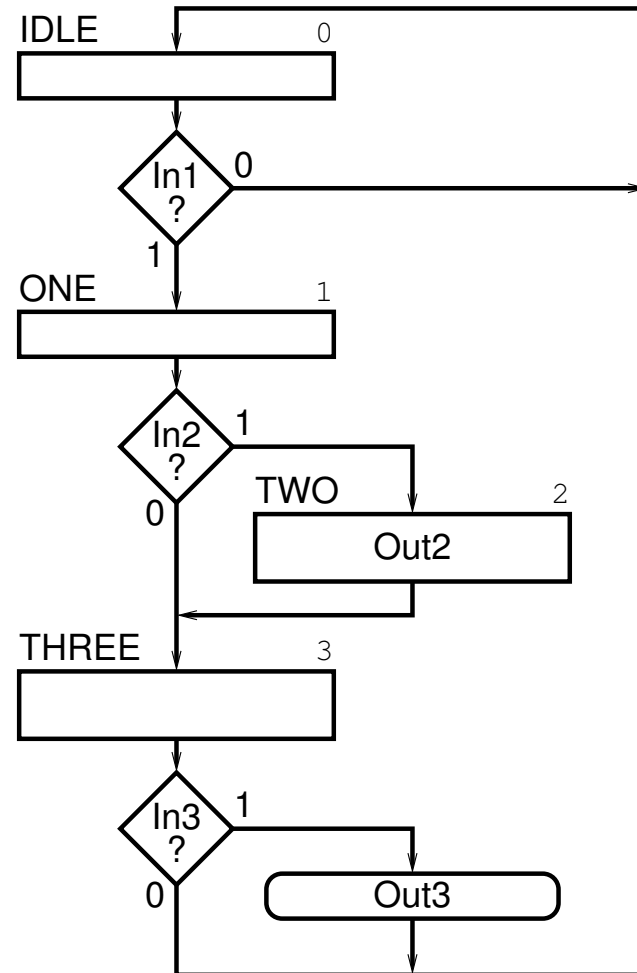


ASM2 – Mealy Machine

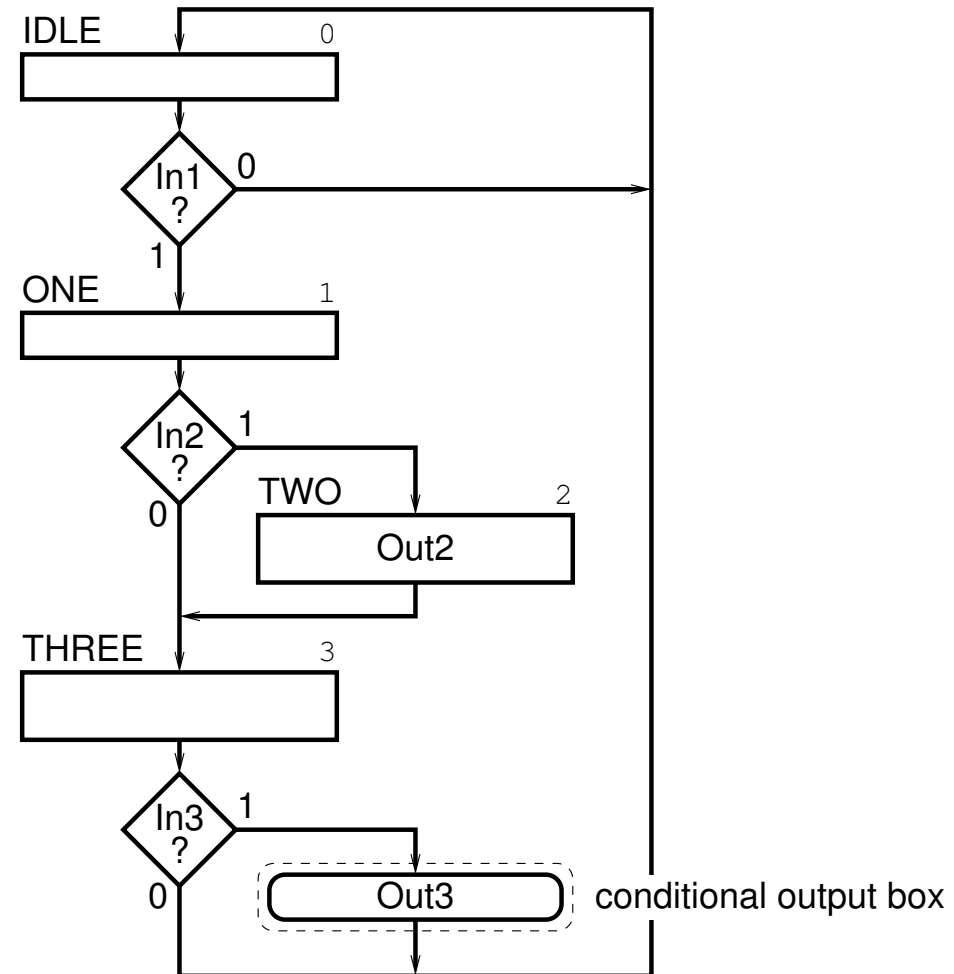


ASM2 – Mealy Machine

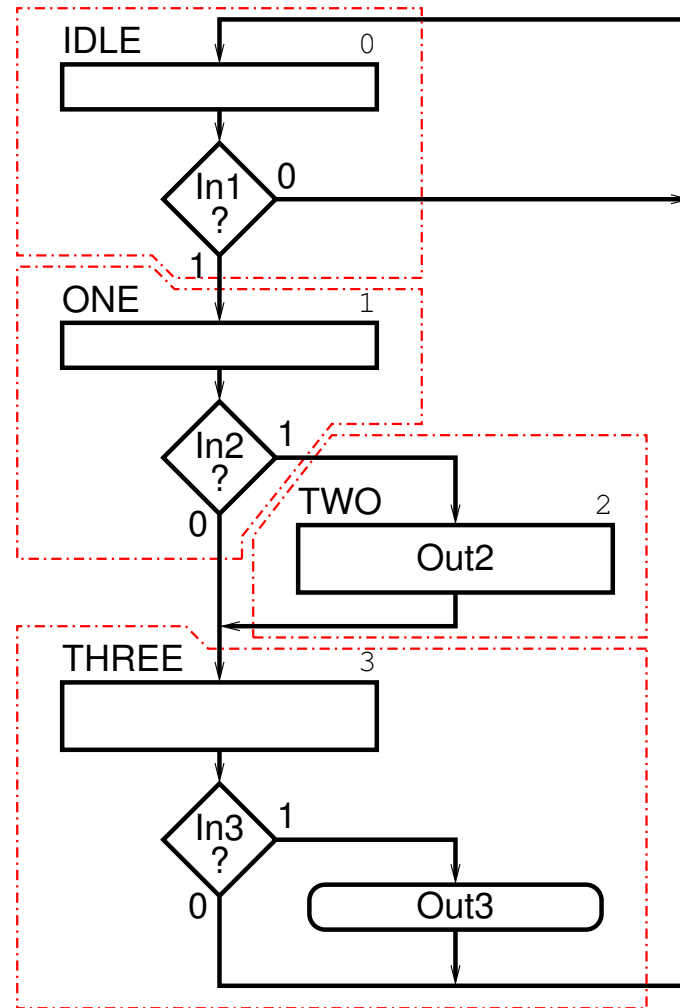

ASM2 – Mealy Machine

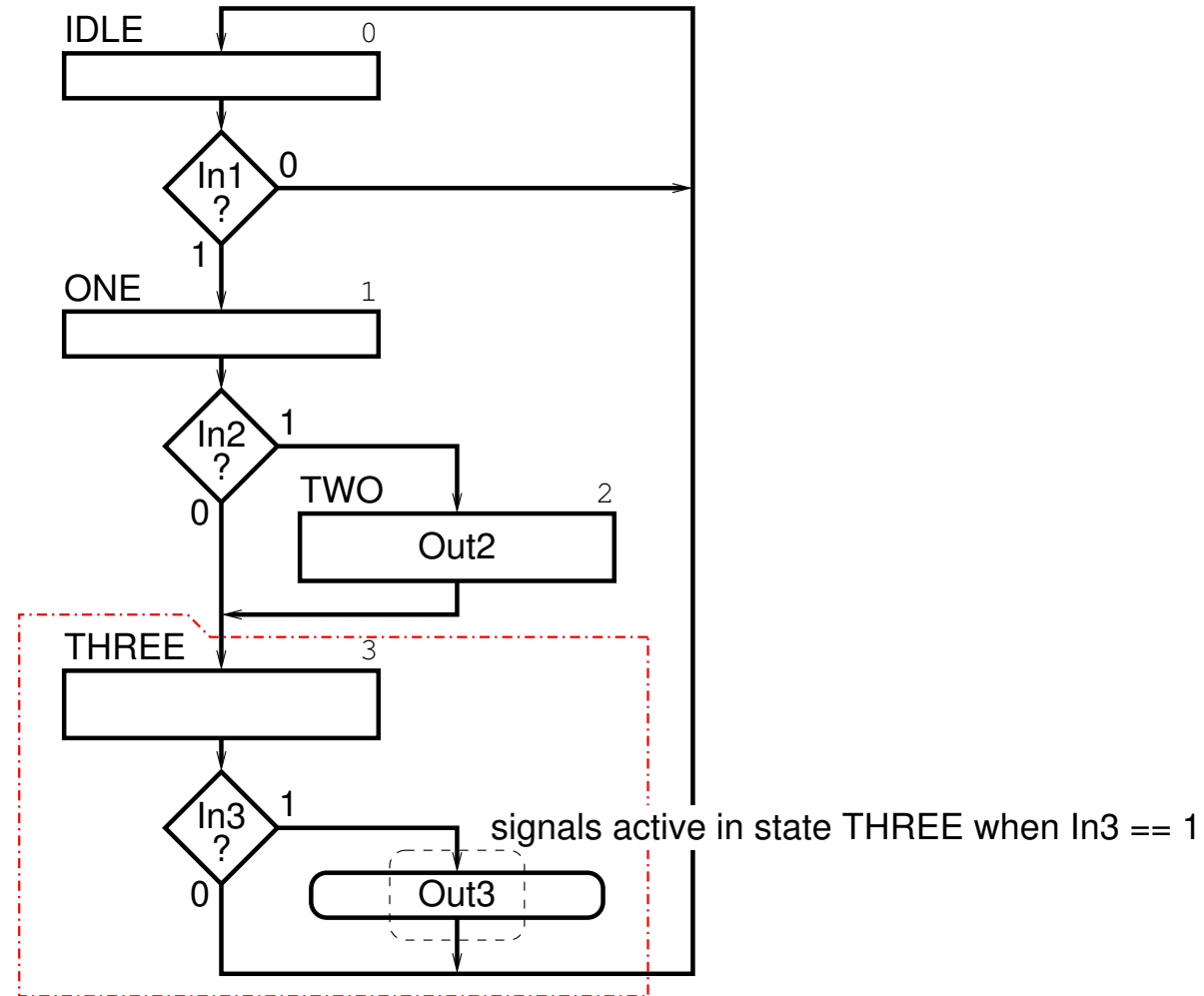

ASM2 – Mealy Machine

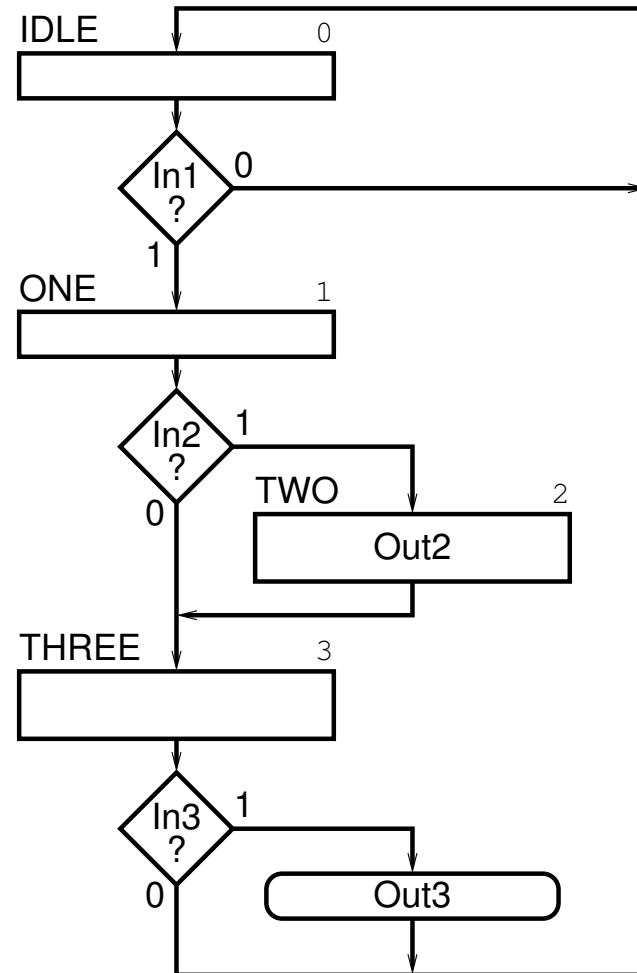

ASM2^a

```
// ----- state declaration -----  
logic [1:0] state;  
  
// ----- state + next state logic -----  
always_ff @(posedge Clock, negedge nReset)  
    if (!nReset)          state <= 0;  
    else  
        case (state)  
            0:          if (In1)  state <= 1;  
            1:          if (In2)  state <= 2;  
                   else          state <= 3;  
            2:          state <= 3;  
            3:          state <= 0;  
        endcase  
  
// ----- output logic -----  
logic Out2, Out3;  
    assign Out2 = (state == 2);  
    assign Out3 = (state == 3) && In3;
```

ASM2^b – using state names

```
// ----- state declaration -----  
enum logic [1:0] { IDLE=0, ONE=1, TWO=2, THREE=3 } state;  
  
// ----- state + next state logic -----  
always_ff @(posedge Clock, negedge nReset)  
    if (!nReset)          state <= IDLE;  
    else  
        case (state)  
            IDLE : if (In1)  state <= ONE;  
            ONE  : if (In2)  state <= TWO;  
                   else      state <= THREE;  
            TWO  :          state <= THREE;  
            THREE:          state <= IDLE;  
        endcase  
  
// ----- output logic -----  
logic Out2, Out3;  
    assign Out2 = (state == TWO);  
    assign Out3 = (state == THREE) && In3;
```

ASM2^c – using a procedural block to infer combinational logic


```
// ----- state declaration -----  
enum logic [1:0] { IDLE, ONE, TWO, THREE } state;  
  
// ----- state + next state logic -----  
always_ff @(posedge Clock, negedge nReset)  
    if (!nReset)          state <= IDLE;  
    else  
        case (state)  
            IDLE : if (In1)  state <= ONE;  
            ONE  : if (In2)  state <= TWO;  
                   else      state <= THREE;  
            TWO  :          state <= THREE;  
            THREE:          state <= IDLE;  
        endcase  
  
// ----- output logic -----  
logic Out2, Out3;  
always_comb  
    begin  
        Out2 = (state == TWO);  
        Out3 = ((state == THREE) && In3);  
    end
```

ASM2^h single procedural block not possible⁷


```
// ----- state block generates Out2 -----  
enum logic [1:0] { IDLE, ONE, TWO, THREE } state;  
logic Out2;  
  
always_ff @(posedge Clock, negedge nReset)  
  if (!nReset) begin state <= IDLE; Out2 <= 0; end  
  else  
    begin  
      Out2 <= (state == ONE) && In2;  
      case (state)  
        IDLE : if (In1) state <= ONE;  
        ONE  : if (In2) state <= TWO;  
              else state <= THREE;  
        TWO  : state <= THREE;  
        THREE: state <= IDLE;  
      endcase  
    end  
  
// ----- output logic generates Out3 -----  
logic Out3;  
  assign Out3 = (state == THREE) && In3;
```

⁷n.b. single procedural block solution not possible for Mealy machine since we have conditional outputs.


Datapath Control

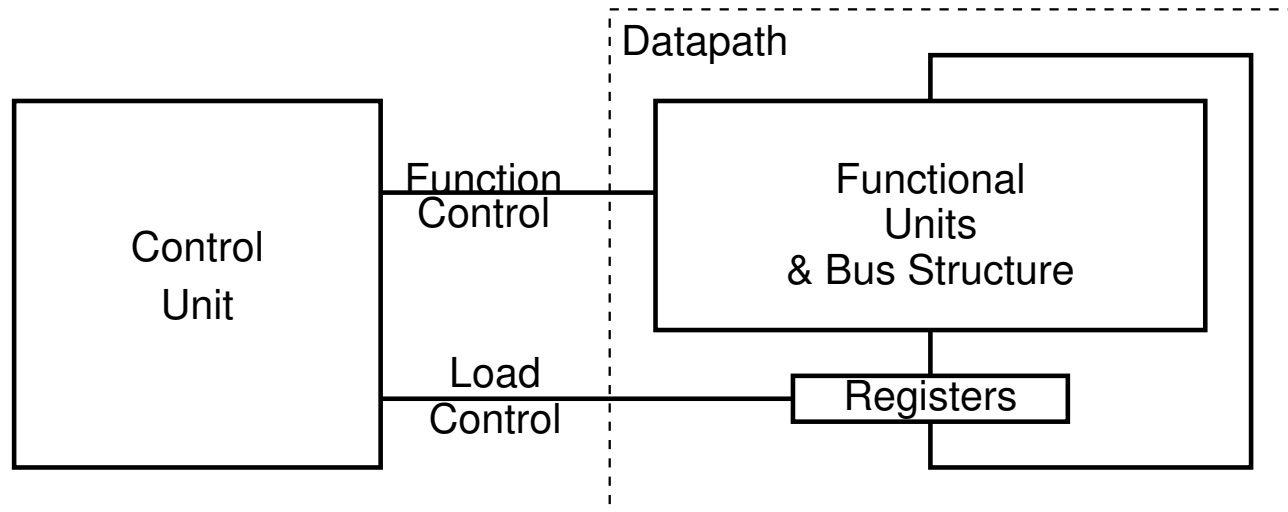

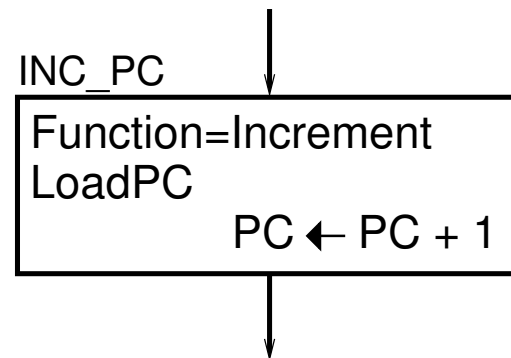For successful update we must simultaneously control function and register update:



Datapath Control

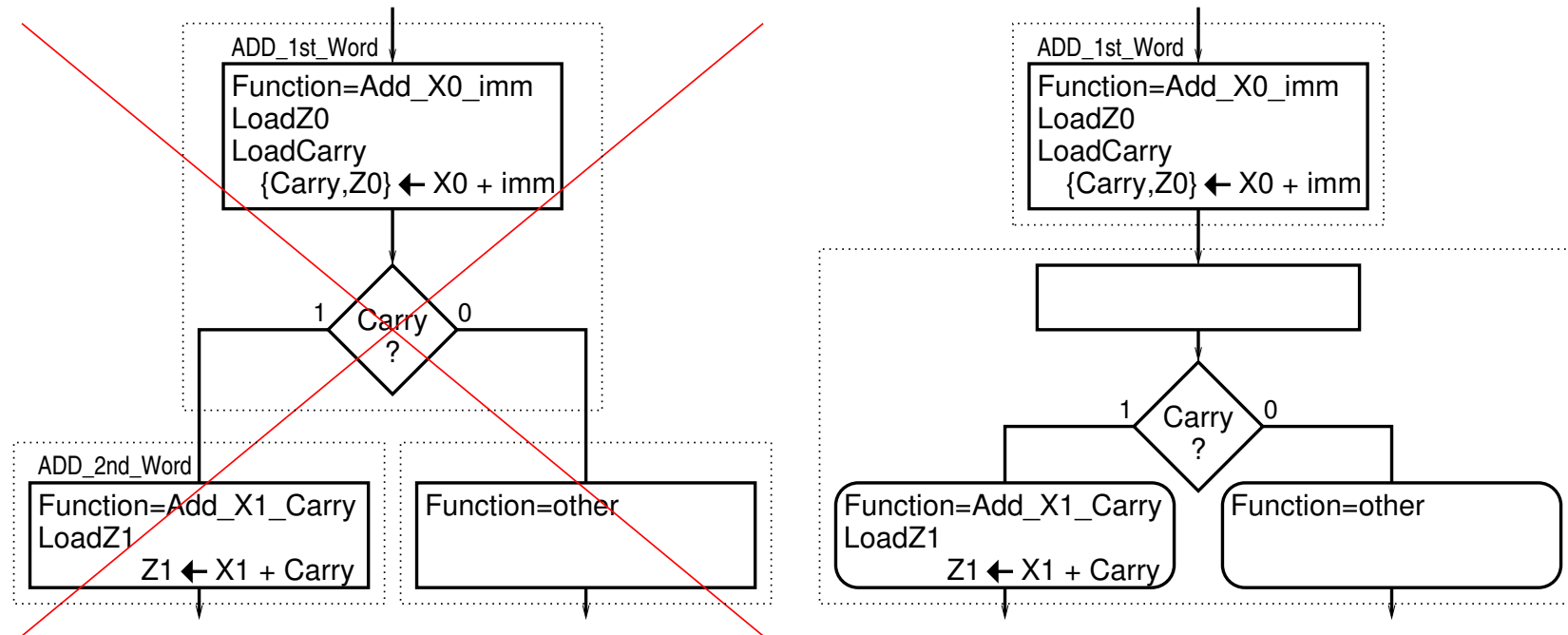

Since datapath registers are updated at the end of the clock cycle, we must wait until the next state before testing new values⁸.

⁸in some cases it may be better to test values at the input to a register, e.g. if (nextCarry == 1)...