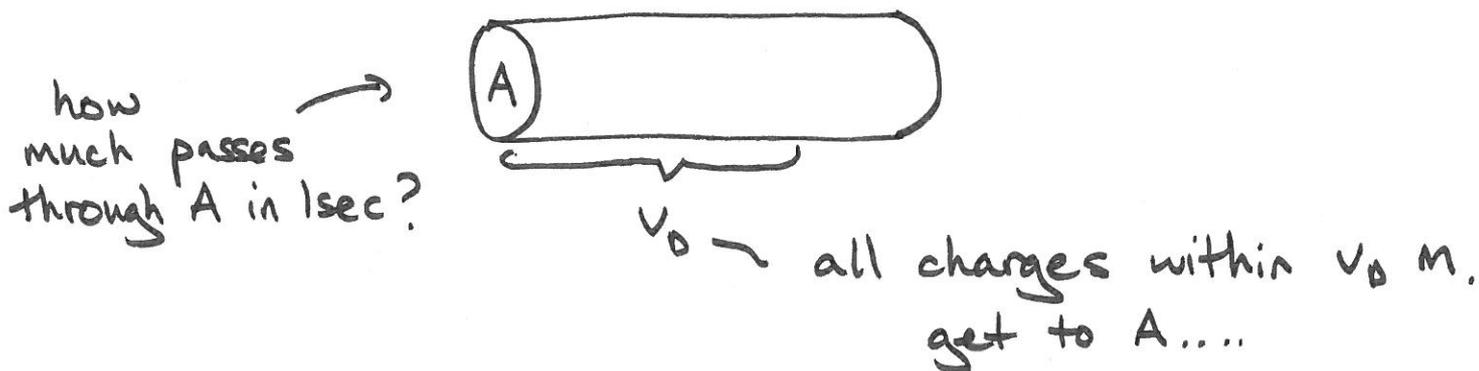


IX ELECTRIC CURRENTS

Charges in an \vec{E} field experience a force & accelerate.

In a wire e^- accelerate, collide with an ion & slow, accelerate again etc. In a constant \vec{E} (due to constant potential difference across wire's ends) a steady state can be reached with constant mean drift velocity \vec{v}_D

Current, I , is charge passing / second



$$I = \frac{\Delta Q}{\Delta t} = n q v_D A$$

\uparrow number density of charges
 \uparrow charge

The current can change... so define instantaneous current as

$$I = \frac{dq}{dt} \quad (\text{ie } \Delta t \rightarrow 0 \text{ limit})$$

I can also vary in space so define a current density

$$\vec{J} = nq \vec{v}_D$$

$$I = \int \vec{J} \cdot d\vec{A}$$

$$\vec{J} \rightarrow \text{circle } dA \quad I = J dA$$

$$\vec{J} \rightarrow \text{circle } dA \quad I = 0$$

Ohm's Law

In normal materials


$$\vec{J} \propto \vec{E}$$

$$\vec{J} = \frac{\vec{E}}{\rho}$$

ρ is resistivity

$\sigma = \frac{1}{\rho}$ conductivity

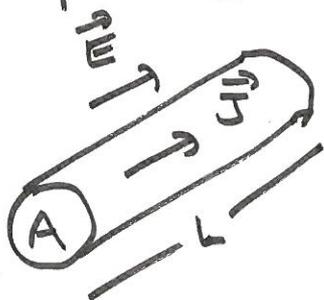This is a microscopic version of Ohm's Law. We can compute from it for a ~~piece~~ resistor



$$\text{p.d.} = V = |\vec{E}| L$$

$$(\phi = -\int \vec{E} \cdot d\vec{l})$$

$$I = JA$$

$$|\vec{J}| = \frac{|\vec{E}|}{\rho} \Rightarrow \frac{I}{A} = \frac{1}{\rho} \left(\frac{V}{L} \right)$$

$$\Rightarrow V = IR, \quad R = \frac{L\rho}{A}$$

← local property of material

↑
property of macroscopic object

Power

If a charge q falls through a potential difference V it acquires energy qV . In steady state all this goes to heating

$$P = \frac{\text{energy}}{\text{sec}} = \frac{dq}{dt} V = IV$$

Circuit Components

Wires

We assume wires are perfect conductors and all points along a wire have the same potential.

Resistors

Resistors have finite ρ and hence $V = IR$

In Series




I is the same through all so we have sequential drops in V , $V_i = IR_i$

$$V_{TOT} = \sum_i V_i = I \sum_i R_i$$

$$\Rightarrow R_{TOT} = R_1 + R_2 + \dots$$

In Parallel

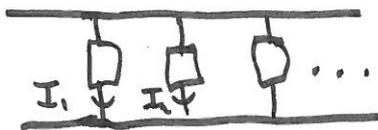

V across each is the same

I_i add


$$I_{TOT} = \frac{V}{R_{TOT}} = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots \right)$$

$$\Rightarrow \frac{1}{R_{TOT}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

Capacitors

We have seen $C = Q/V$

In Series

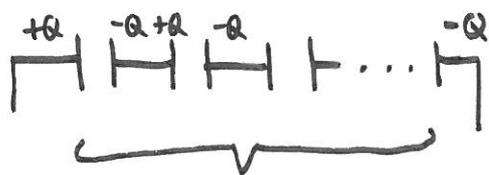


charge conservation
places same Q on each
plate

$$V = V_1 + V_2 + \dots$$

$$\frac{1}{C_{TOT}} = \frac{V_{TOT}}{Q} = \frac{V_1 + V_2 + \dots}{Q} = \sum_i \frac{V_i}{Q}$$

$$\Rightarrow \frac{1}{C_{TOT}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$

In Parallel

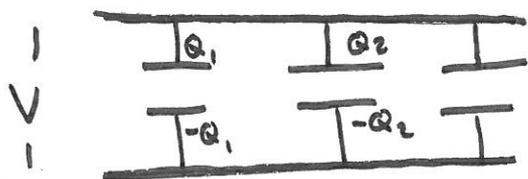


All the plates make one
effective capacitor storing
total charge $\sum_i Q_i$

$$C_{TOT} = \frac{Q_{TOT}}{V} = \frac{Q_1 + Q_2 + \dots}{V} = \sum_i C_i$$

$$C_{TOT} = C_1 + C_2 + \dots$$

Batteries

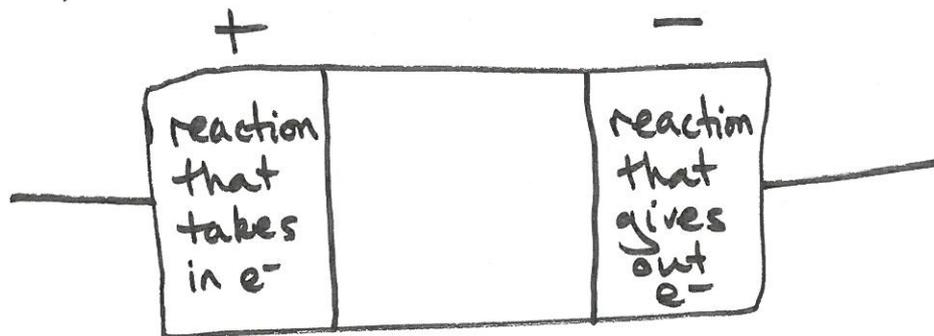The idea is to separate two chemical reactions that would occur together - one needs e^- from the other.





If the two ends are connected e^- run between the two ends allowing both reactions to go. Without the energy is chemically stored.

eg Car Battery

- VE
TERMINAL



+ VE
TERMINAL

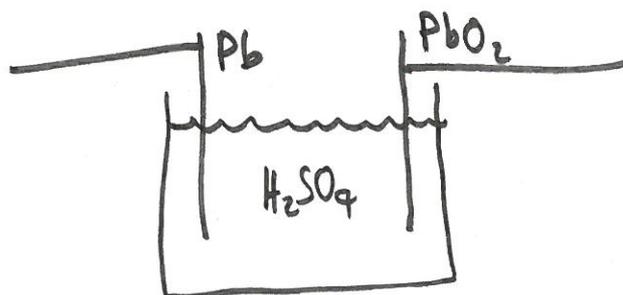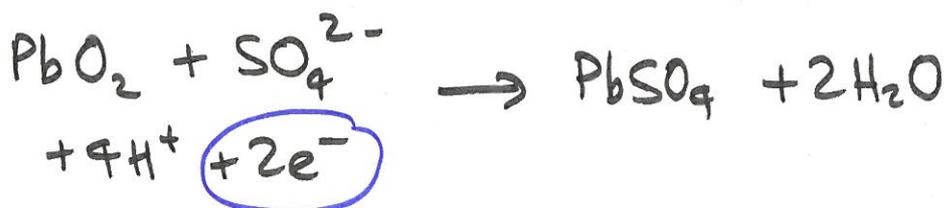

Kirchhoff's Laws

(i) Charge is conserved - at any point in a circuit

$$\sum I_{\text{incoming}} = 0$$



If this weren't true then charge would accumulate at the point.


(ii) Potential is single valued so if you go round a loop

$$\oint_{\text{round loop}} \vec{E} \cdot d\vec{l} = 0$$

\Rightarrow in a circuit

$$\sum_{\text{any loop}} V_i = 0$$

eg RC Circuit

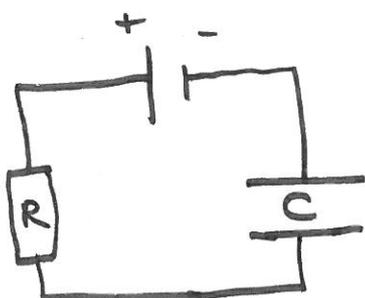


$$V_R + V_C = V_S$$

$$IR + Q/C - V_S = 0$$

$$R \frac{dQ}{dt} + Q/C - V_S = 0$$

eg charging a capacitor

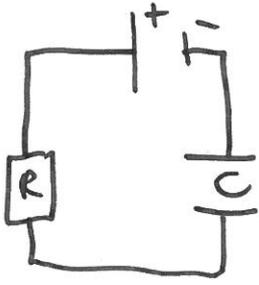

$$IR + Q/C = V_s$$

diff w.r.t t:

$$\frac{dI}{dt} R + \frac{I}{C} = 0$$

$$\frac{dV_s}{dt} = 0$$

Over any short period $\frac{dI}{I} = - \frac{dt}{RC}$


We can sum both sides over some period as long as we make the limits match

$$\int_0^t - \frac{dt}{RC} = \int_{I(t=0)=I_0}^{I(t=t)=I} \frac{dI}{I}$$


$$-\frac{t}{RC} = \ln \frac{I}{I_0}$$

$$\Rightarrow I = I_0 e^{-t/RC}$$

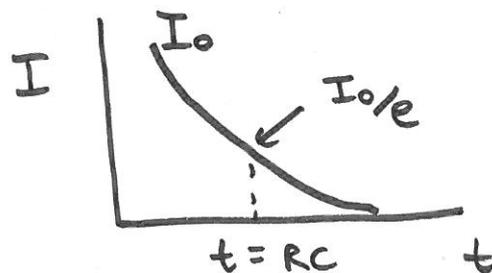The current falls exponentially as charge grows on the plates resisting the current.



eg Discharging a capacitor

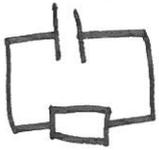

$$IR + \frac{Q}{C} = 0$$

$$\frac{dQ}{dt} R + \frac{Q}{C} = 0$$

$$\int_{Q_0}^Q \frac{dQ}{Q} = - \int_0^t \frac{dt}{RC}$$

$$\ln Q/Q_0 = -t/RC$$

$$Q = Q_0 e^{-t/RC}$$

The charge on the plates falls exponentially with characteristic time RC again.