

The need for testing

- Real systems may have manufacturing defects. Short circuits, missing components, damaged components etc.
- Need to know if a system (board, IC, whole system) has a defect (and therefore doesn't work). Don't want to sell bad systems - don't want to reject good systems.
- ∴ Need for testing is economic.

Two approaches

- Functional testing - does system work correctly?
- Structural testing - does system contain a fault?
- Functional testing can imply a long and difficult task!

Fault Models

- Fault Modelling
 - What Defects occur?
 - How can they be modelled?
 - What do models imply?

PCB Defects

- Breaks in connections
 - bad etching
 - stress
- Short Circuits
 - solder flow
- Bad solder joints

IC Defects

- Open Circuits
 - electromigration
 - current overstress
 - corrosion
- Short Circuits
- Incorrect Transistor Action
 - silicon or oxide defects
 - mask misalignment
 - impurities
 - gamma radiation
- "Latch-up"
 - transient currents
- Data Corruption
 - alpha particles
 - EMI

How do defects manifest themselves?

- Static failures (50%)
 - shorts, breaks etc
- Dynamic failures (49%)
 - out of spec components
 - timing failures
- Intermittent failures (1%)
 - environmental

Fault Model

- Physical Defect manifests itself as a logical fault
 - Applies only to digital circuits
 - (No analogue fault models.)
- Stuck Fault Model
 - Many physical defects can be modelled as a circuit node being:
 - stuck at 1 (s-a-1)
 - stuck at 0 (s-a-0)

Single-Stuck Fault Model

- Assumptions:
 - The fault directly affects only one node
 - The node is stuck at either 0 or 1
- These assumptions make test pattern generation easier
- Validity of Single-Stuck Fault Model?
 - Multiple faults do occur
 - Can multiple faults mask each other?
 - Number of faults might rise with complexity
 - Can all defects be modelled with stuck fault model?
 - The model appears to be valid most of the time
 - Almost all test pattern generation relies on this model
 - Multiple faults are found with test patterns for single faults


Fault-oriented Test Pattern Generation

- Prepare a fault list (e.g. all nodes stuck-at 0 & stuck-at 1)
repeat
 - write a test
 - check fault cover (one test may cover > 1 fault)
(delete covered faults from list)until fault cover target is reached
1. Test pattern generation (writing a test) may be random or optimised. Ideally we want a minimum number of tests - cheaper to apply!
 2. One test may cover more than one fault, often faults are indistinguishable.
 3. If we simply want a pass/fail test, we can remove faults from further consideration, once we have found a test for a fault. If we want to diagnose a fault (for subsequent repair) we probably want to find all tests for a fault to deduce where the fault occurs.
 4. Fault cover target may be less than 100%. The higher the cover, the greater the number of tests and hence the cost of applying the test.

Testability

- How testable is a system?
 - a. Controllability - can we control all the nodes to establish if there is a fault?
 - b. Observability - can we observe and distinguish between a faulty node and a correct node?

Sensitive Path Algorithm

 


- 7 nodes, \therefore 14 stuck faults:
 - a/0, a/1, b/0, b/1, c/0, c/1, d/0, d/1, e/0, e/1, f/0, f/1, z/0, z/1
 - "a stuck-at-0" etc.
- To test for a/0, need to set a to 1 (fault-free condition).
- Need to observe existence or otherwise of fault at z.
- If b is 0, e is 1 irrespective of a. \therefore b must be 1.
- Similarly if f is 1, z is 1, irrespective of e, \therefore f must be 0.
- Thus we are establishing a sensitive path from a to z.
- To force f to 0, either c or d or both must be 0.

- If the fault $a/0$ exists, e is 1, z is 1. If the fault does not exist, e is 0, z is 0.
- We can conclude from this that a test for $a/0$ is $a=1, b=1, c=0, d=1$, for which the fault-free output is $z=0$. This can be expressed as 1101/0. Other tests are 1110/0 and 1100/0. Therefore, there is more than one test for the fault $a/0$.
- To test for $e/1$, requires that $f=0$ to make e visible at z . $\therefore c$ or d or both must be 0. To make $e=0$ requires that $a=b=1$. So a test for $e/1$ is 1101/0. This is the same test as for $a/0$! So one test can cover more than one fault.

Algorithm


1. Select a fault;
 2. Set up inputs to force the node to a fixed value;
 3. Set up inputs to transmit node value to an output;
 4. Check for consistency;
 5. Check for coverage of other faults;
- The aim is to find the minimum number of tests that cover all the possible faults. 100% fault cover may not be possible.
 - Fan-out and reconvergence can cause difficulties for this algorithm. Improved algorithms (D-algorithm, PODEM) use similar techniques but overcome drawbacks.

Undetectable Faults

 

- Consider the function $z = a.c + b.\bar{c}$
- To avoid hazards, the redundant term may be included:
 $z = a.c + b.\bar{c} + a.b$
- To test for f/0, $f=1$, $\therefore a=b=1$
- To transmit to z, $d=e=0$.
- For $e=0$, $b=0$ and/or $c=1$.
- For $d=0$, $a=0$ and/or $c=0$.
- Thus there is an inconsistency!
- Untestable faults are due to redundancy.

Fault simulation

 

- One test pattern can be used to find more than one potential fault.
- For example, suppose we wish to detect if node E is stuck at 0 ($E/0$).
- $E/0$ cannot be distinguished from $G/0$ or $A/0$ or $B/0$.
- In all these cases, G will be 1 normally and 0 in the presence of one of these faults.
- Hence, the input pattern $A = 1, B = 1, C = 0, D = 0$ can be used to detect four possible faults.
- As there are 7 nodes in the circuit, there are 14 possible stuck-at faults.
- This pattern covers 4 faults and it can be shown that of the 16 possible input patterns, 6 are sufficient to detect all the possible stuck-at faults in the circuit.

Testing Sequential Circuits

- Testing combinational circuits is relatively easy, provided, there is no redundancy in the circuit. Number of test vectors $\ll 2$ (no. of inputs)
- Testing sequential circuits is difficult because circuits have states. May require long sequences of inputs to reach states. Some faults may be untestable, because certain states cannot be reached.
- N.B. All sequential circuits **MUST** have a set or reset to initialise all flip-flops or testing is nearly impossible.