Finding an Euler Path

$$Z = \overline{(A+B+C)\bullet(D+E)\bullet F}$$

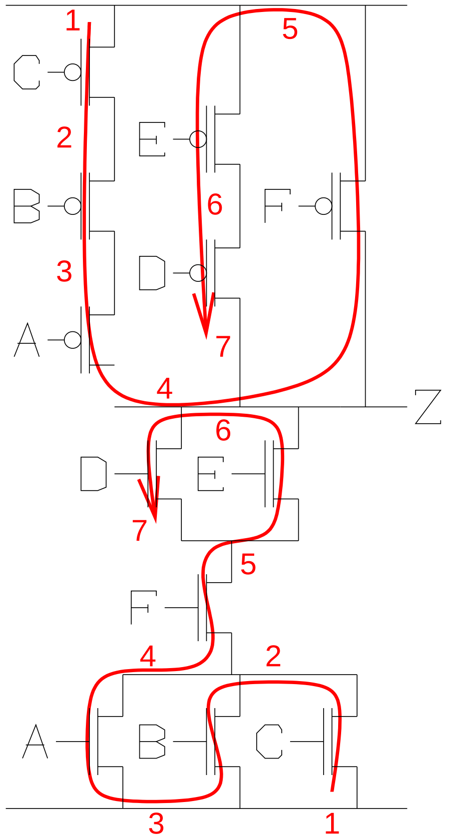

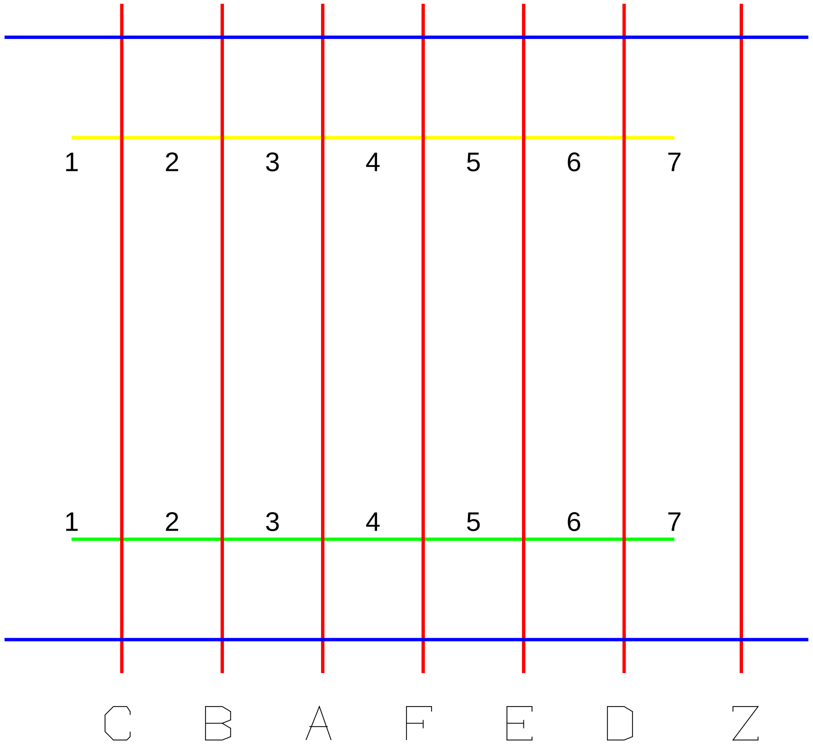

Finding an Euler Path

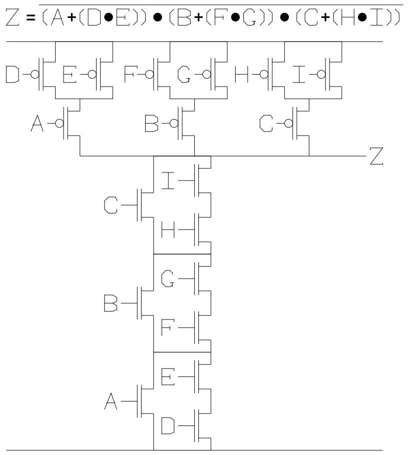

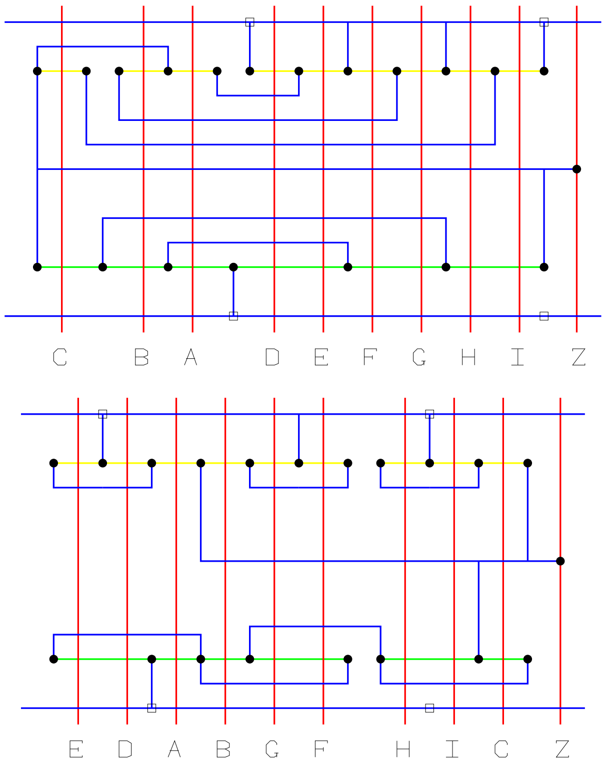

No possible path through p-transistors.
No re-arrangement will create a solution!