Latches and Flip-Flops

- CMOS transmission gate latch

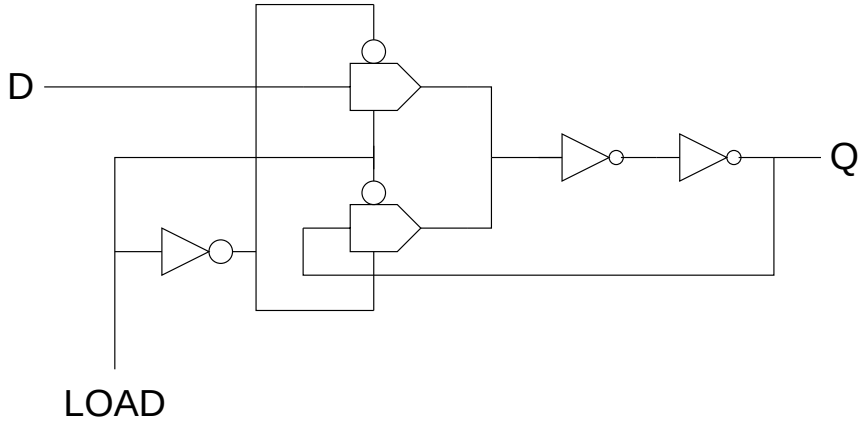

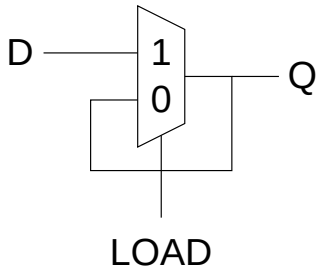

A simple transparent latch can be build around a transmission gate multiplexor

- transparent when load is high
- latched when load is low
- two inverters are required since the transmission gate cannot drive itself

Latches and Flip-Flops

- Transmission gate latch layout

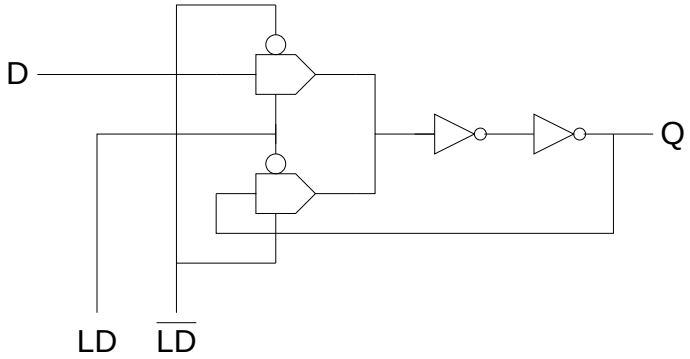

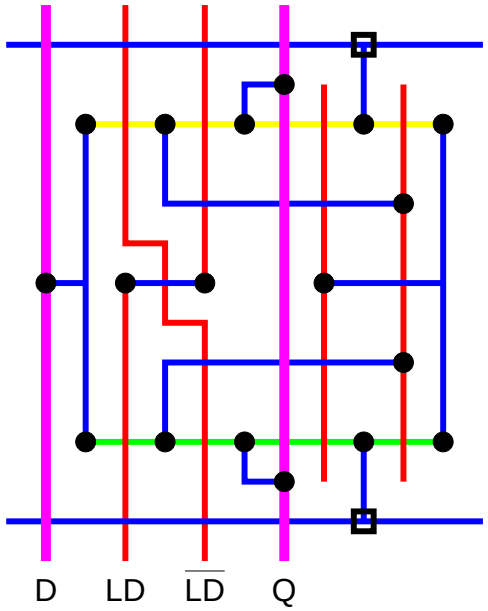

– a compact layout is possible using 2 layer metal

Latches and Flip-Flops

- A simpler layout may be achieved using tristate inverters.

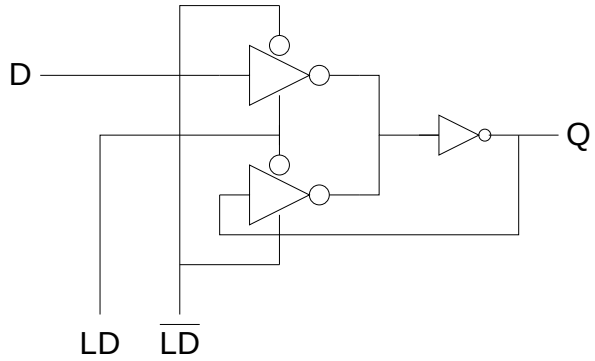

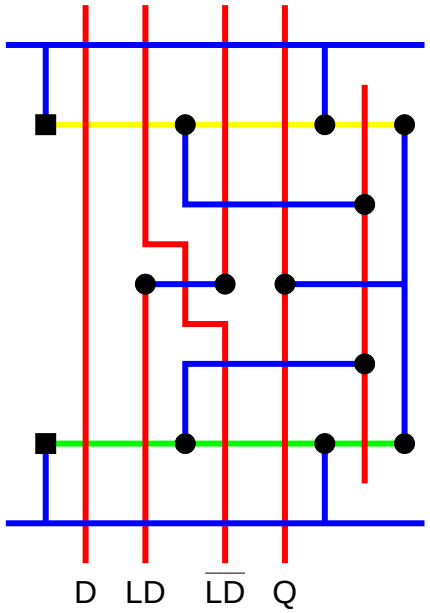

  - this design requires two additional transistors but may well be more compact.

Latches and Flip-Flops

- For use in simple synchronous circuits we use a pair of latches in a master slave configuration.

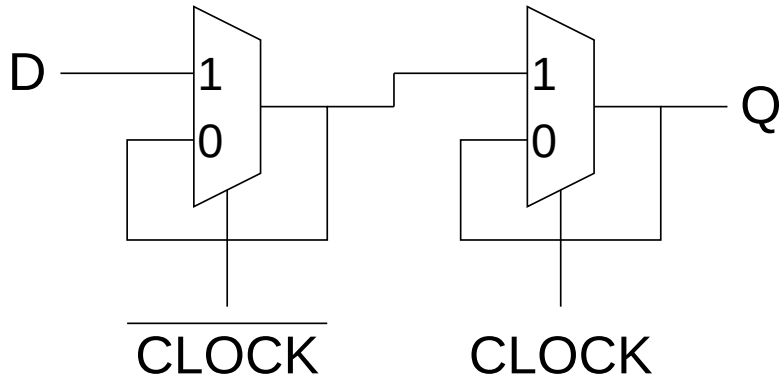

  - this avoids the race condition in which a transparent latch drives a second transparent latch operating on the same clock phase.
  - the circuit behaves as a rising edge triggered D type flip-flop.

Latches and Flip-Flops

- Transmission gate implementation

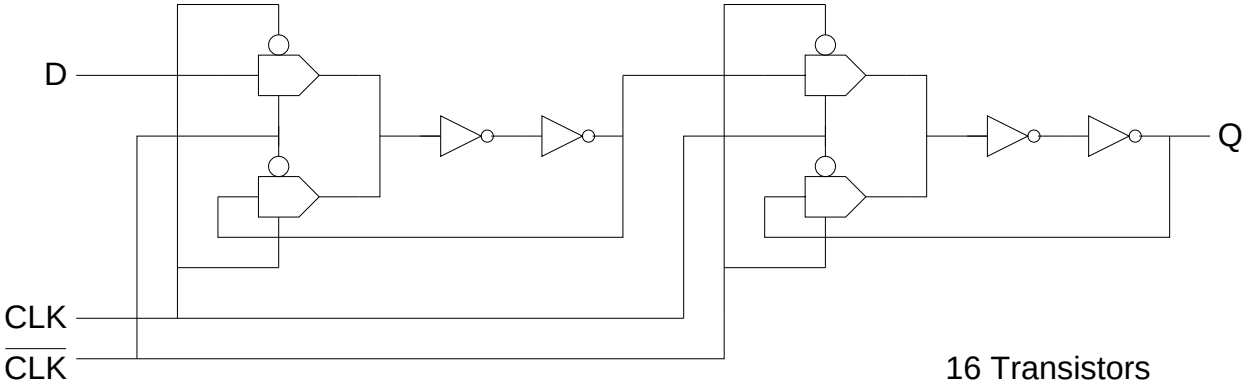

16 Transistors

- Tristate inverter implementation

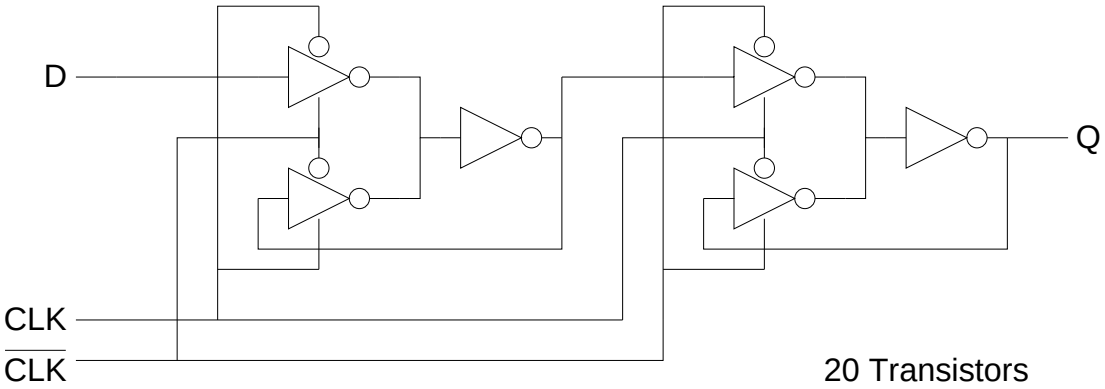

20 Transistors

Latches and Flip-Flops

- Alternative configuration

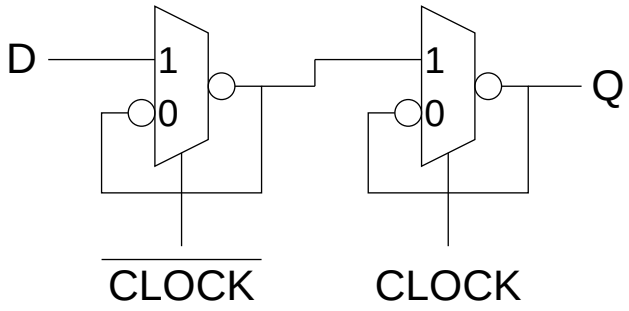

– Implementation

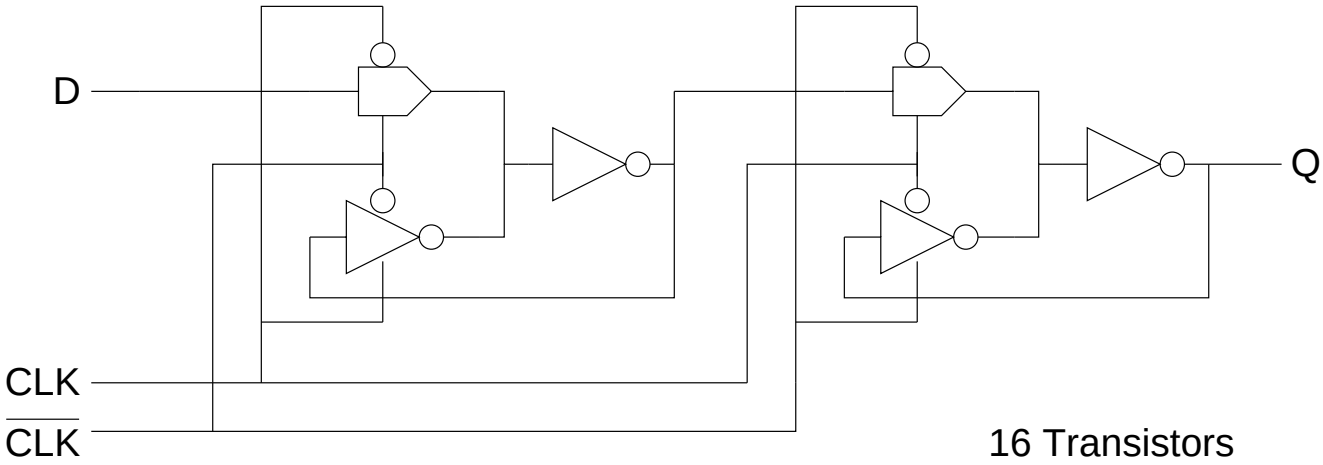

16 Transistors

Latches and Flip-Flops

- Layout of master slave D type.

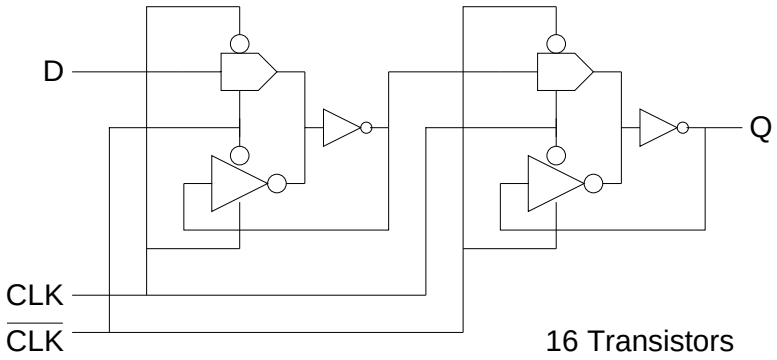

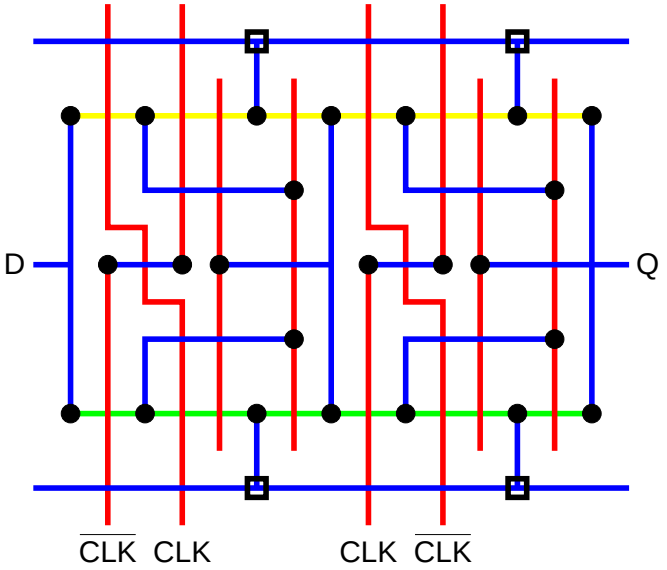

  - very compact using alternative configuration.

Latches and Flip-Flops

- For the same functionality we could use an edge triggered D type:

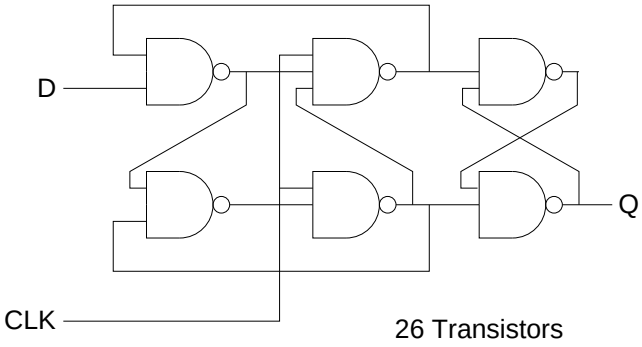

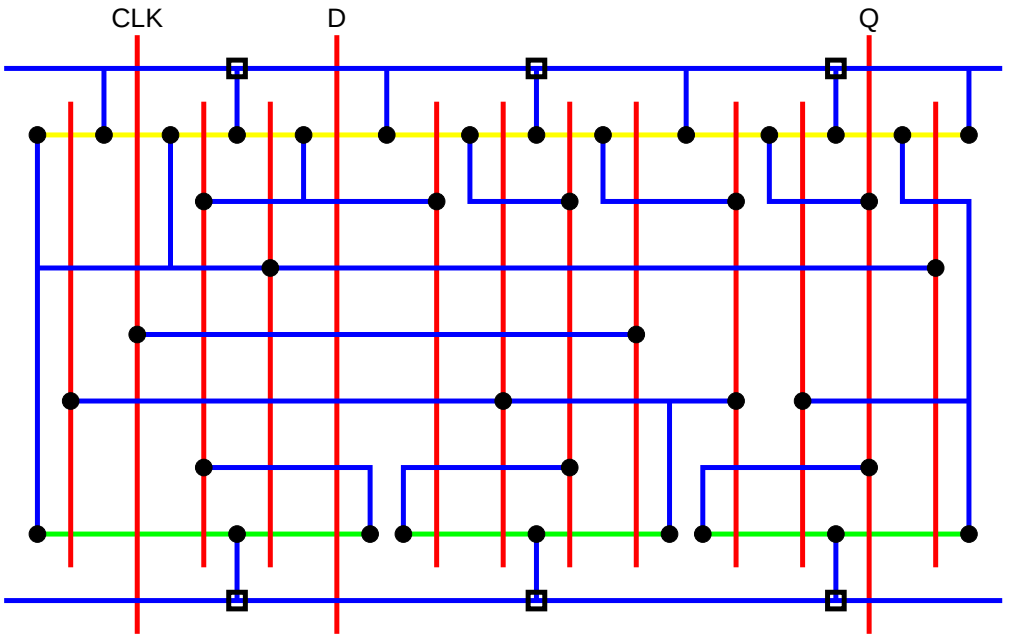

  - a few more transistors
  - more complex wiring
  - simpler clock distribution

Register File

Where we have large amounts of storage the use of individual latches can lead to space saving.

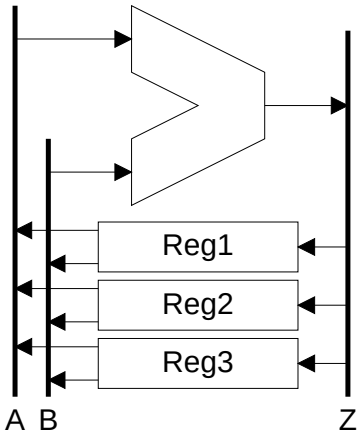

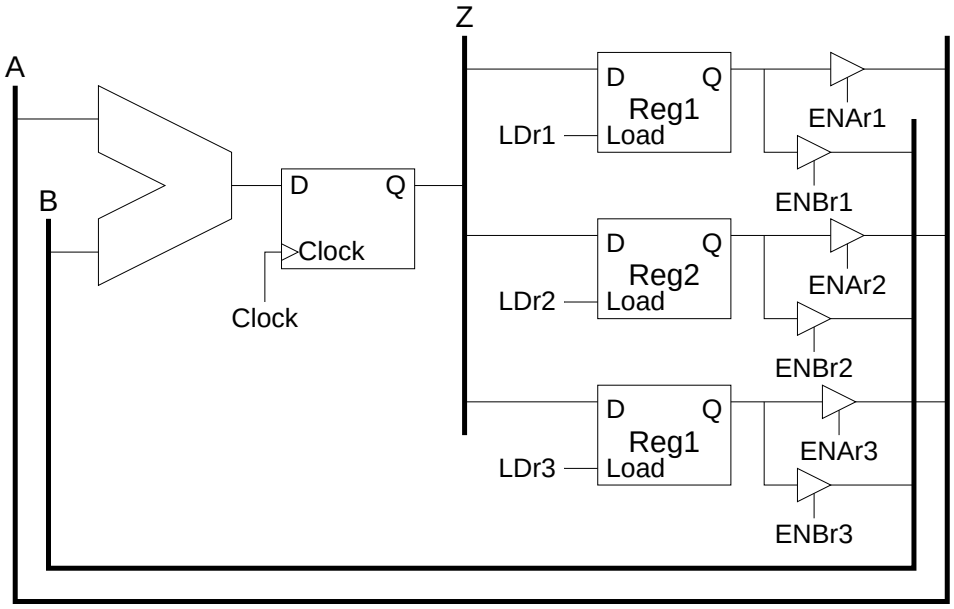

- Load signals must be glitch free with tightly controlled timing.
- Edge Triggered D-type prevents a race condition ($Reg1 \leftarrow Reg1 + Reg2$).